

27/06/19

Chapter - 3 : NETWORK THEOREMS :

Lecture 1 : INTRODUCTION OF THEVENIN'S THEOREM :

Purpose of learning Network Theorems :

To simplify the network parameters very easily & with less number of steps.

3.1 Thevenin's Theorem :

1. This theorem is valid for both independent and dependent sources n/w's.
2. Equivalent of thevenin's n/w is same as practical voltage equivalent n/w. The practical voltage equivalent n/w is given as


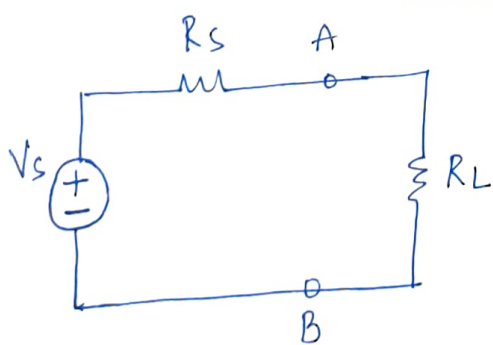
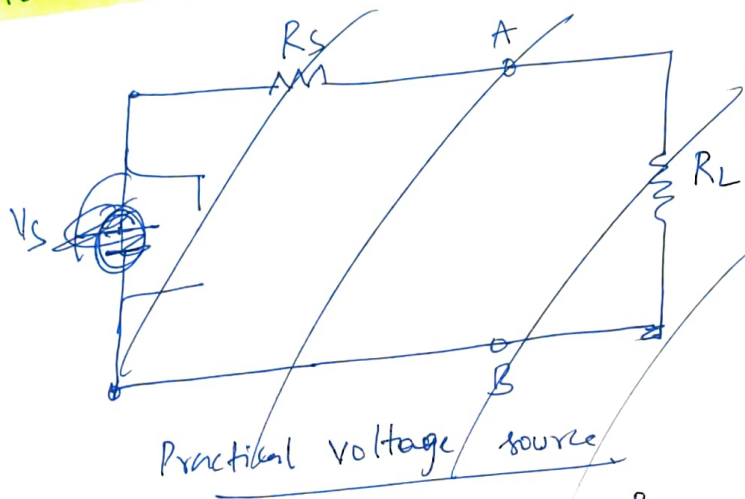


Fig: Practical Voltage Source equivalent

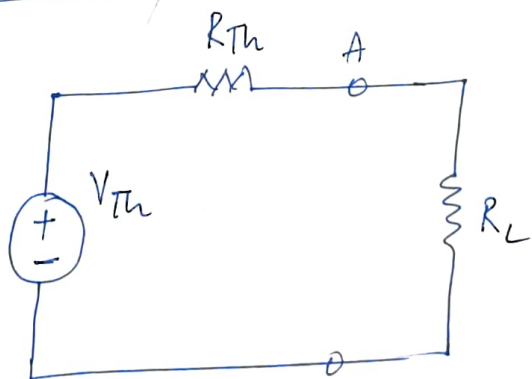

Equivalent ckt of Thevenin

3. Thevenin voltage is referred as open ckt voltage across the load terminal, i.e., current across the load terminal is '0' (zero).


i.e. $V_{OC} = V_{TH}$

$$V_{TH} = V_{OC} = \text{ideal Voltmeter reading } (V_m)$$

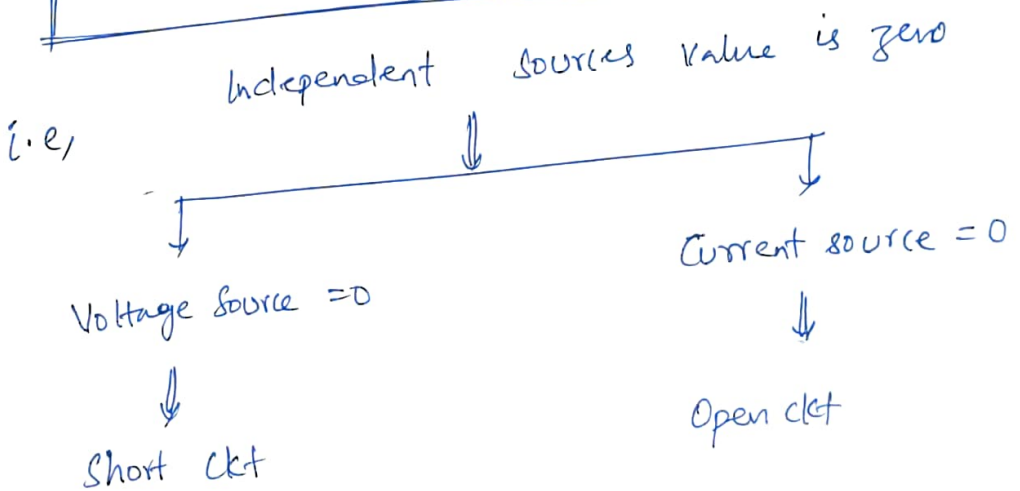4. Calculation of R_{TH} depends on the behaviour of the network.

4 a) When n/w contains only independent sources then

$$R_{TH} = R_{eq} \text{ across the load terminal with all independent sources value is zero}$$



$$R_{TH} = R_{eq} \text{ when voltage source is short ckt circuit (or) current source is open ckt}$$

4b) When n/w contains both dependent and independent sources

$$R_{Th} = \frac{V_{dc}}{I_{dc}} \quad \left| \begin{array}{l} \text{when independent sources value is zero, which} \\ \text{means voltage source is S.C \& current source} \\ \text{is O.C} \end{array} \right.$$

where V_{dc} = dc voltage across the load terminal.

I_{dc} = dc current which flowing from V_{dc} .

4c) When n/w contains only dependent source :

$$R_{Th} = \frac{V_{dc}}{I_{dc}}$$


↓
no conditions.

→ special case of n/w

$$V_{Th} = 0 \text{ volt}$$


$$V_{Th} = (\text{function of independent sources})$$

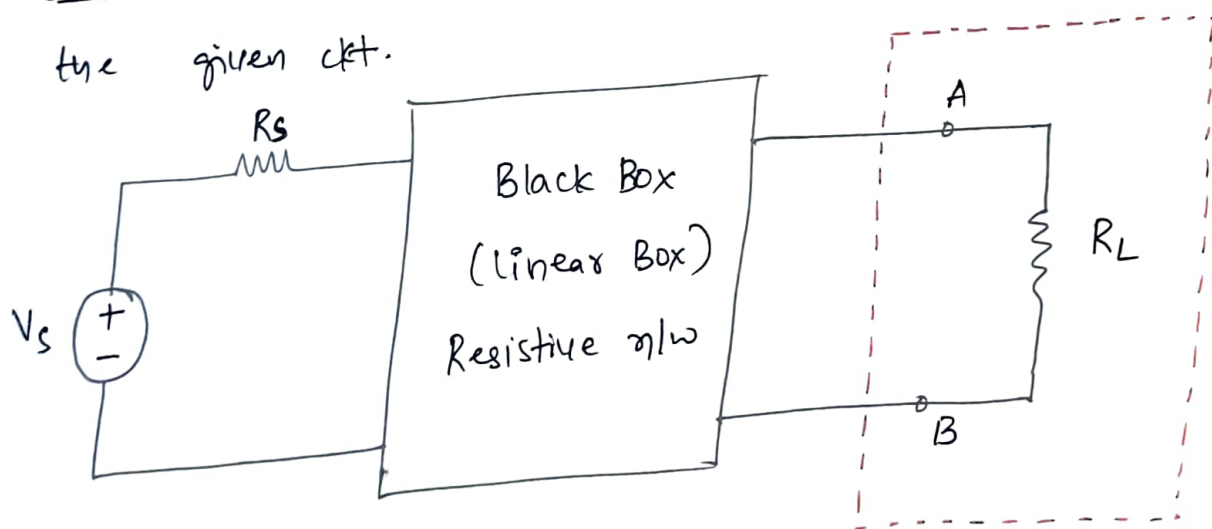Example: find the thevenin eq of the dotted part of the given ckt.



soln: Let us consider the dotted part of the given n/w.

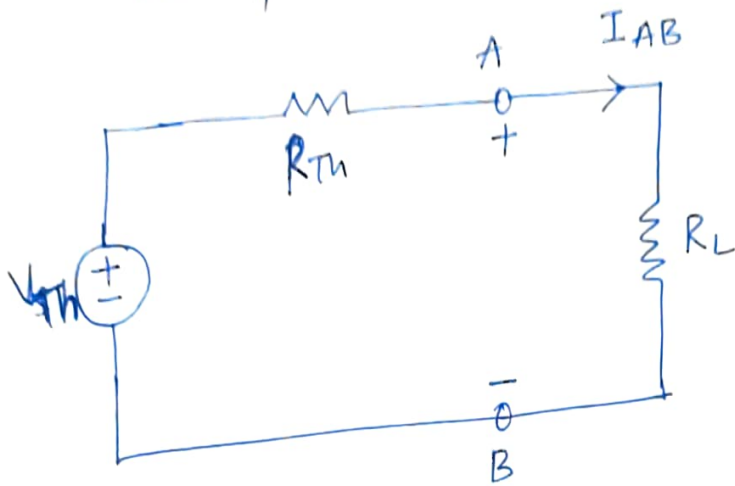Thevenin equivalent of the dotted part of n/w is as follows



Applying KVL for loop ABA

$$V_{Th} - I_{AB} R_{Th} - I_{AB} R_L = 0$$

$$V_{Th} = I_{AB} (R_{Th} + R_L).$$

$$I_{AB} = \frac{V_{Th}}{R_{Th} + R_L} \rightarrow \textcircled{1}$$

We know by Ohm's law

$$V_{AB} = I_{AB} R_L = \frac{V_{Th} R_L}{R_{Th} + R_L}$$

$$V_{AB} = \frac{V_{Th} R_L}{R_{Th} + R_L} \rightarrow \textcircled{2}$$

Conclusion:

1. If we know thevenin voltage (V_{Th}) & thevenin resistance (R_{Th}) of the given n/w, we can find the load current & load voltage of that particular

n/w. This is the main intention or essence of the thevenins theorem.

2: We can find voltage & current of any branch of n/w if we know thevenins voltage & thevenins resistance of the n/w.


Lecture-2

Example Based On Thevenins Theorem (1) :

Example: Consider the given n/w below

(i) find the thevenin equivalent across 'AB'

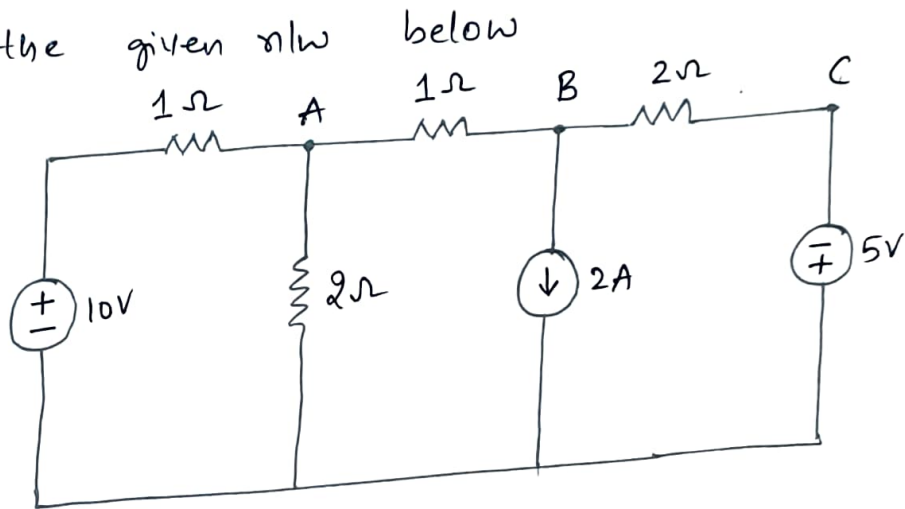(ii) find the thevenin equivalent across 'BC'



Soln: (i) Thevenin Equivalent Across AB :


Now (I) To find V_{Th} :

Consider thevenin eqⁿ across AB.

According to the property -


→ Remove the branch resistance across AB. (Open ckt)

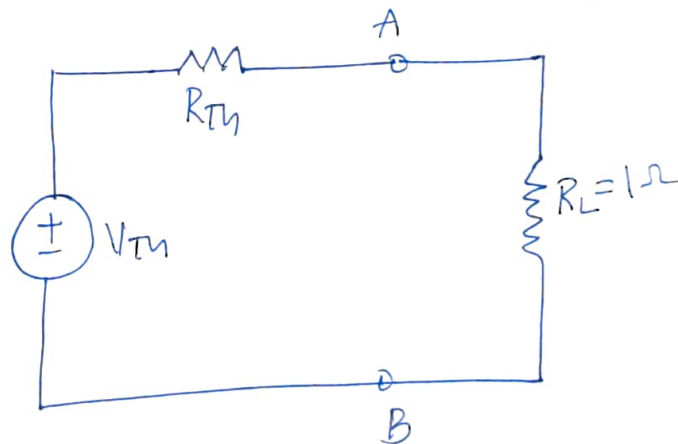→ Find the voltage across AB (i.e. V_{AB}). It is also called as open ckt voltage



$$V_{AB} = V_{oc} = V_{Th}$$

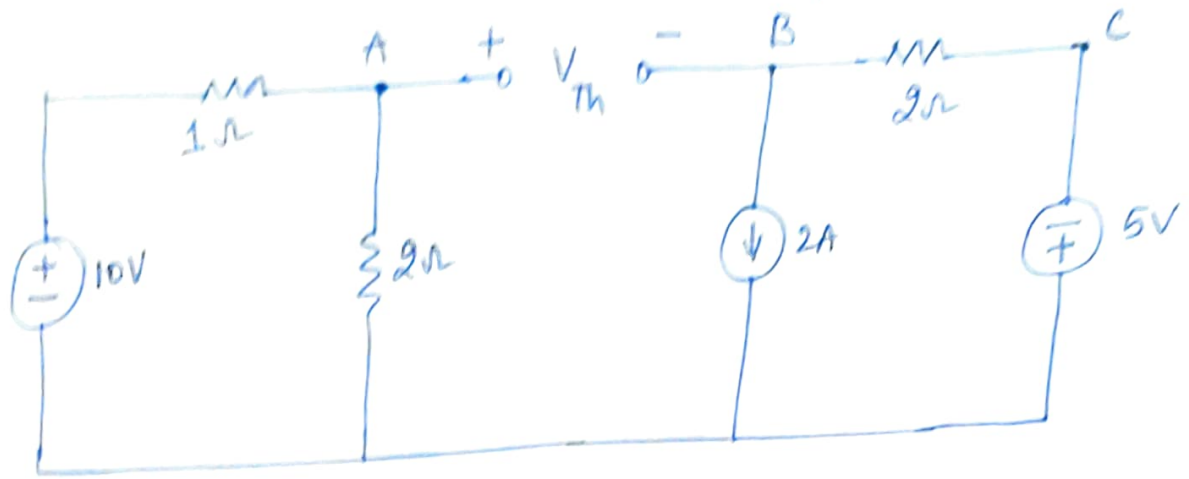I_{AB} is known as Thevenin voltage ^{at} ~~across~~ AB.



$$V_{AB} = V_{Th} = V_A - V_B.$$

(a) V_A :

By VDR $V_A = \frac{2}{3} \times 10 = \frac{20}{3} \text{ volts}; \quad \boxed{V_A = \frac{20}{3} \text{ volts}}$

(b) V_B :

~~By KVL $\rightarrow 5 + (V_B \times 2)$~~

By KCL at 'B'

$$\frac{V_B + 5}{2} + 2 = 0$$

$$\frac{V_B + 5 + 4}{2} = 0$$

$$\boxed{V_B = -9 \text{ volts}}$$

$$\boxed{V_{Th} = V_{AB} = \frac{20}{3} + 9 = \frac{47}{3} \text{ volts}}$$



To find R_{Th} :

Here we observe only independent sources. So

we have to use first case

i.e. $R_{Th} = R_{eq}$

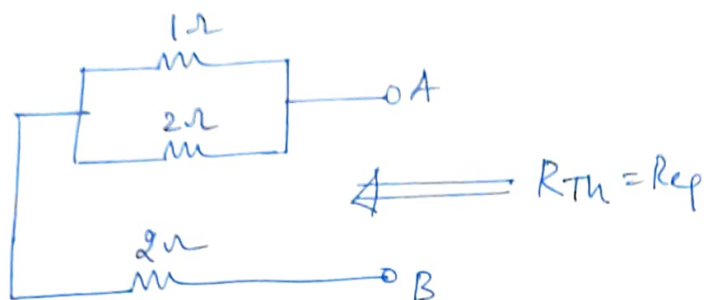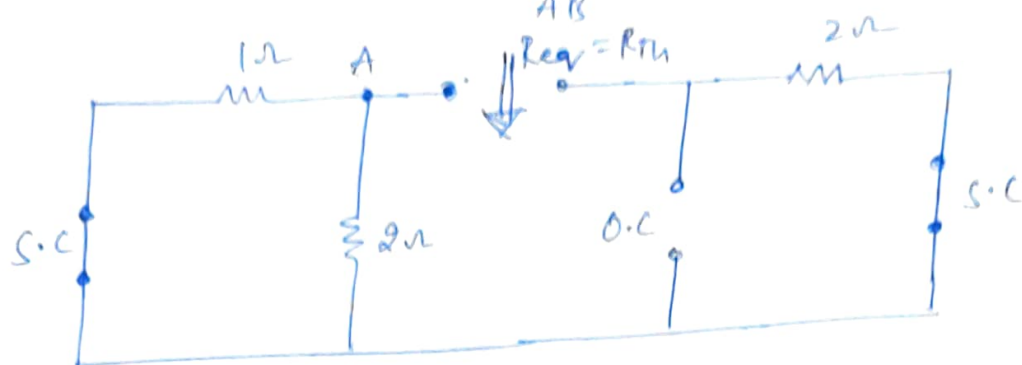
when voltage sources are S.C
& current sources are O.C



$$R_{Th} = (1 || 2) + (2) = \left(\frac{1 \times 2}{1+2} \right) + (2) = \frac{2}{3} + 2 = \frac{8}{3} \Omega$$

$\therefore R_{Th} = \frac{8}{3} \Omega$

Thevenin eq across AB :

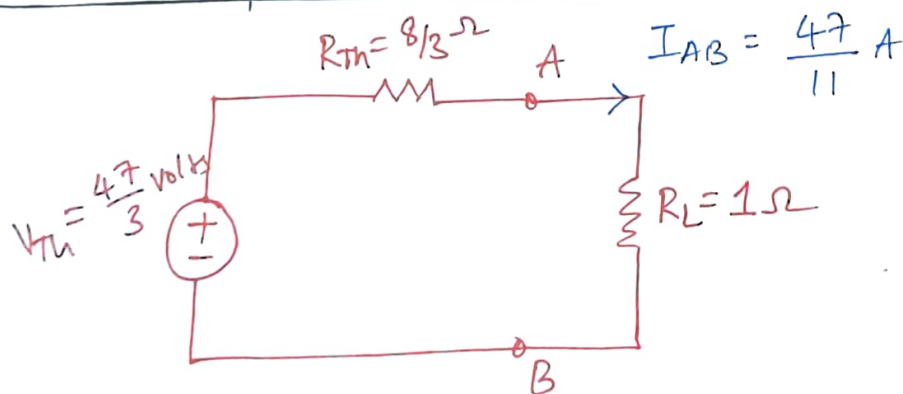

$I_{AB} = ?$

$$\frac{47}{3} - I_{AB} \times \frac{8}{3} - I_{AB} \times 1 = 0$$

$$I_{AB} \left[1 + \frac{8}{3} \right] = \frac{47}{3} \Rightarrow I_{AB} \left[\frac{11}{3} \right] = \left[\frac{47}{3} \right]$$

$$I_{AB} = \frac{47}{11} \text{ A}$$

$$V_{AB} = I_{AB} \times R_L = \frac{47}{11} \times 1 = \frac{47}{11} \text{ volts}$$

$$\therefore V_{AB} = \frac{47}{11} \text{ volts}$$


NOTE:

→ We can find I_{AB} using nodal analysis also.
 → But here we've used thevenin's theorem to find


I_{AB} .


→ Both methods can be used according to the convenience of student.

(ii) Thevenin's Equivalent across BC:

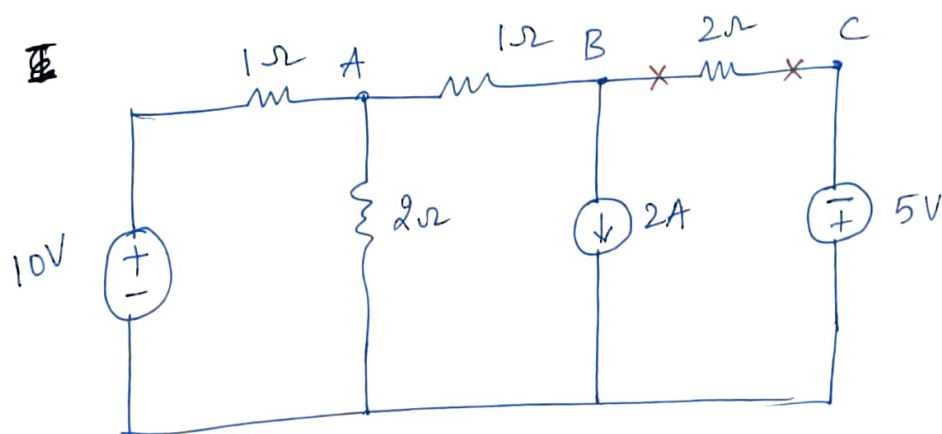

(I) To find V_{th} :

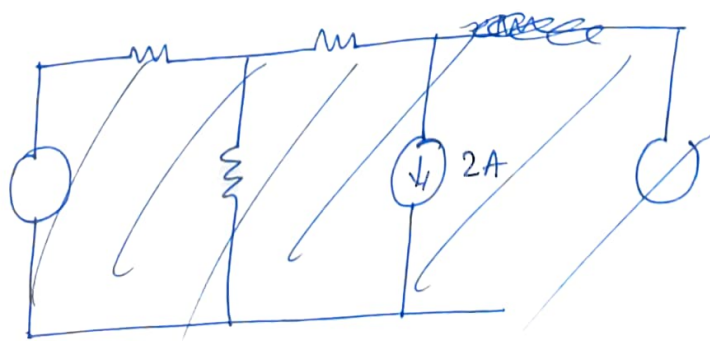

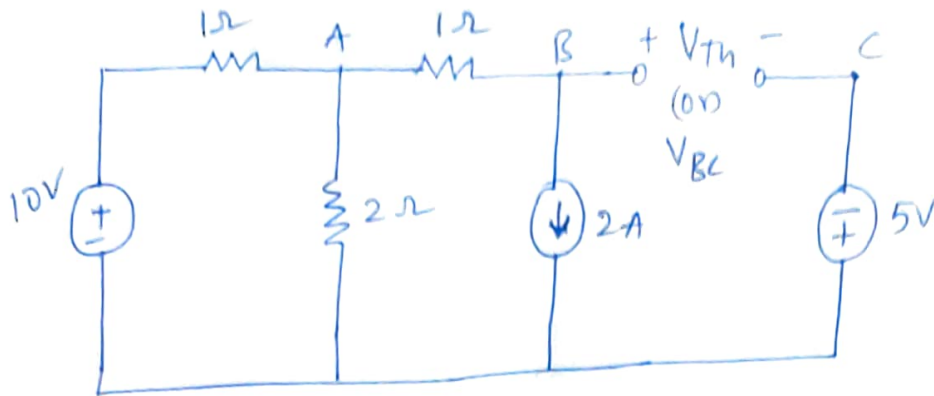

By applying nodal analysis at 'A'.

$$\left(\frac{V_A - 10}{1} \right) + \left(\frac{V_A}{2} \right) + \left(\frac{V_A - V_B}{1} \right) = 0$$

$$2.5 V_A - V_B = 10 \longrightarrow (1)$$

By applying nodal analysis at 'B'

$$\frac{(V_B - V_A)}{1} + 2 = 0$$

$$V_A - V_B = 2 \longrightarrow (2)$$

Solving (1) & (2)

$$1.5 V_A = 8 \Rightarrow V_A = \frac{8 \times 10}{15} = \frac{8 \times 2}{3} = \frac{16}{3}$$

$$\therefore V_A = \frac{16}{3} \text{ volts} \longrightarrow (3)$$

$$V_B = V_A - 2 = \frac{16}{3} - 2 = \frac{16 - 6}{3} = \frac{10}{3} \text{ volts}$$

$$\therefore V_B = \frac{10}{3} \text{ volts} \longrightarrow (4)$$

We have from ckt



$$\therefore V_C = -5 \text{ volts} \longrightarrow (5)$$

$$V_{Th} = V_{BC} = V_B - V_C = \frac{10}{3} + 5 = \frac{25}{3} \text{ volts} \longrightarrow (6)$$

II To find R_{Th} :

The given ckt consists only independent sources.
We have to use 1st case, i.e.,

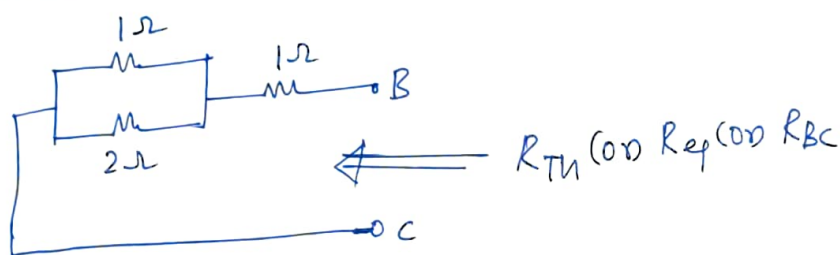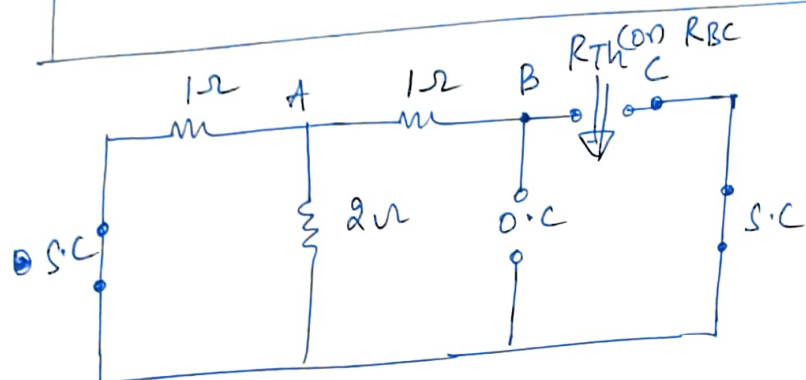
$$R_{Th} = R_{eq} \text{ at BC when Voltage source is S.C. and current source is O.C.}$$



$$R_{Th} = (1 \parallel 2) + 1 = \frac{2}{3} + 1 = \frac{5}{3} \Omega$$

$$\therefore R_{Th} = \frac{5}{3} \Omega$$

Theremins eq. across BC:

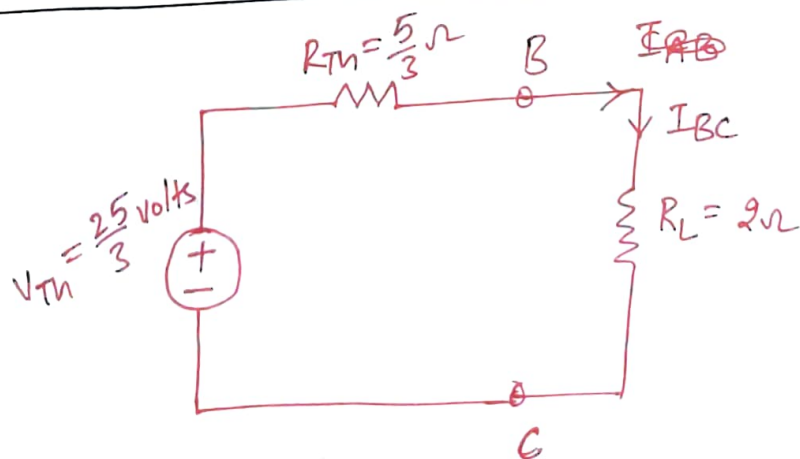

Applying KVL in above loop

$$\frac{25}{3} - \left(I_{BC} \times \frac{5}{3} \right) - (I_{BC} \times 2) = 0$$

$$I_{BC} \left(2 + \frac{5}{3} \right) = \frac{25}{3}$$

$$I_{BC} \left[\frac{11}{3} \right] = \frac{25}{3}$$

$$I_{BC} = \frac{25}{11} \text{ A}$$

from ohms law

$$V_{BC} = I_{BC} \times R_L$$

$$V_{BC} = \frac{25}{11} \times 2 = \frac{50}{11} \text{ volts}$$


$$\therefore V_{BC} = \frac{50}{11} \text{ volts}$$

Lecture-3 :


Example Based On Thevenins Theorem (2)

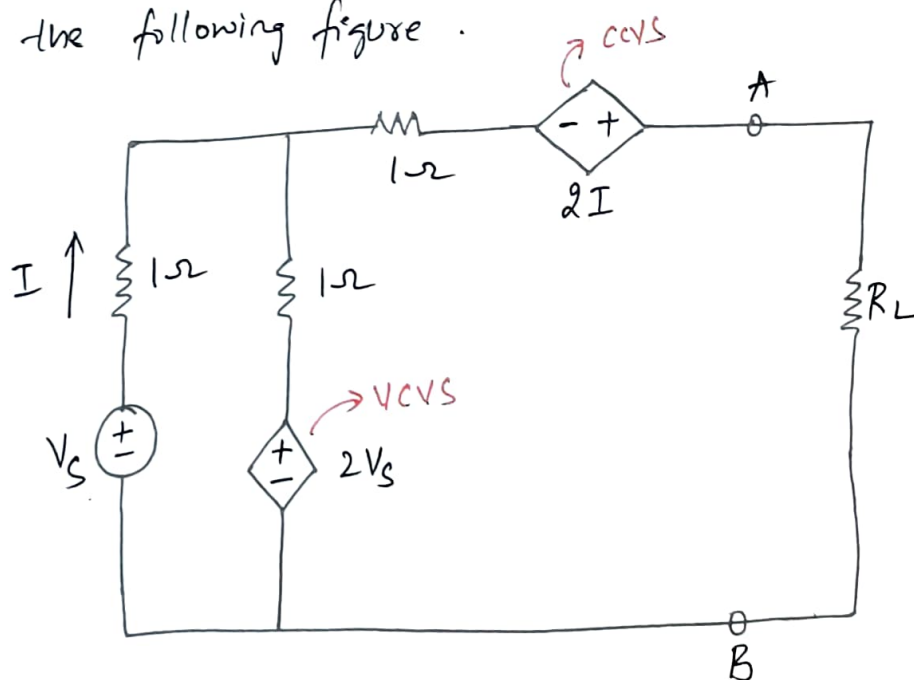Example: Consider the following figure .


find the thevenins
eg. i.e. thevenin
voltage (V_{Th}) &
thevenin resistance
(R_{Th}) across the
terminal AB ?



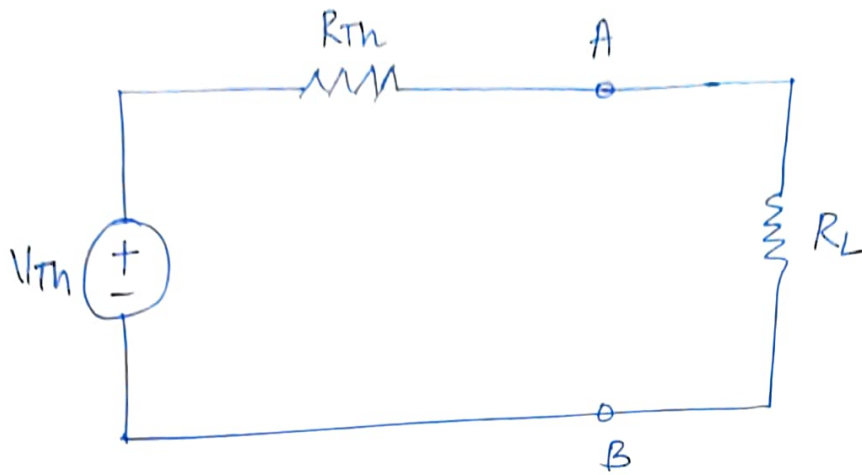sol. The thevenin eq. of given ckt across AB is



Now To find V_{th} !

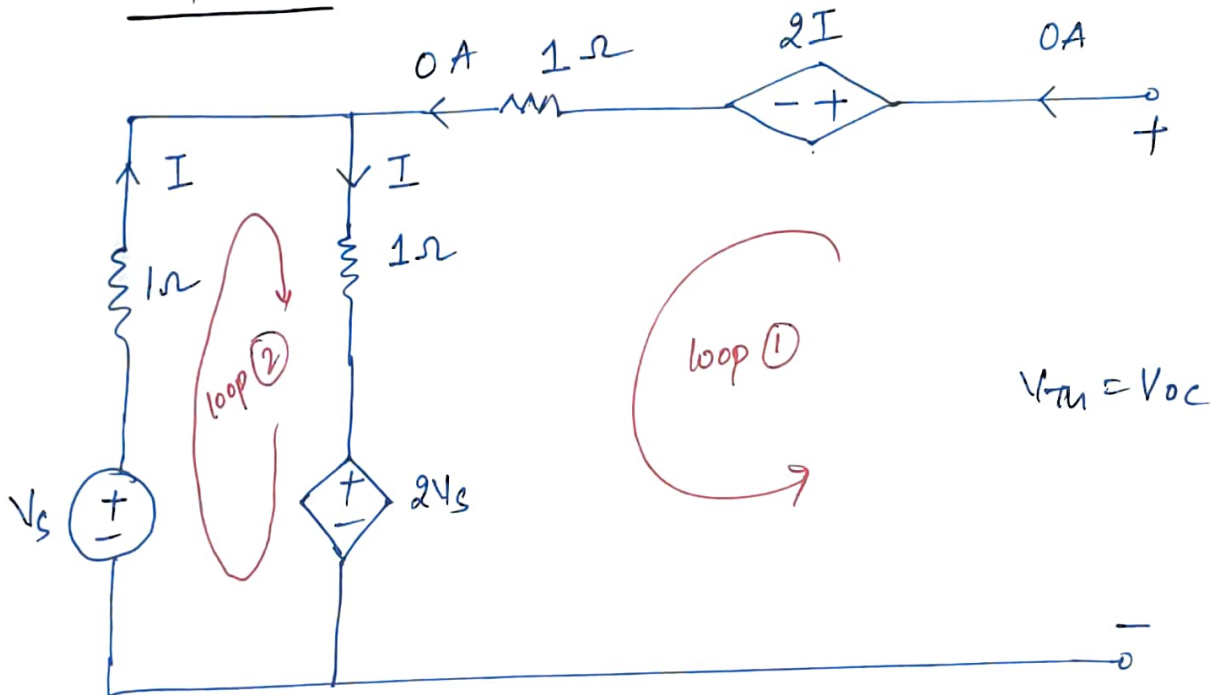

Applying KVL in the loop ①..

$$V_{Th} - 2I - I - 2V_s = 0$$

$$V_{Th} = 2V_S + 3I \longrightarrow (1)$$

Apply KVL in loop (2)

$$V_S - I - I - 2V_S = 0$$

$$-V_s - 2I = 0$$

$$V_S = -2I \rightarrow \text{Circuit diagram showing a voltage source } V_S \text{ and a current } I \text{ through a resistor } R.$$

$$V_S = -2I$$

$$I = \frac{-V_S}{2} \rightarrow (2)$$

put (2) in (1)

$$V_{Th} = 2V_S + 3\left[\frac{-V_S}{2}\right]$$

$$V_{Th} = 2V_S - \frac{3V_S}{2} = \frac{V_S}{2}$$

$$\therefore V_{Th} = \frac{V_S}{2} \text{ volts}$$

NOTE:

finding the V_{Th} is in same style for both (only independent sources) & (combination of independent & dependent sources).

Steps to find V_{Th} :

1. Open the branch which is our area of interest & find the voltage across that particular branch.
2. i.e., open circuit voltage is to be evaluated for the branch which is our area of interest. It is equal to V_{Th} (Thevenin voltage).

$$V_{Th} = V_{oc}$$

To find R_{Th} :

Steps to calculate R_{Th} in a n/w with both independent & dependent sources:

Step-1: Remove the branch b/w the terminals where R_{Th} is to be evaluated.

Step-2: Place the dc voltage ' V_{dc} ' across the terminals where R_{Th} is to be evaluated.

Step-3: Let " I_{dc} " current be flown ~~to~~ from the dc voltage ' V_{dc} '.

Step-4: Make the independent sources value as '0' i.e. 0 for a voltage an independent ~~source~~ voltage source apply (S.C) on it.
i.e. for an independent current source apply

(O.C) on it. (or remove)

Step-4: Do not disturb[?] any dependent source.
Note that any dependent sources must not be removed.

Step-5: For in some special cases, like if the variable in dependent sources depends on the variable of independent sources;

In that case that particular ~~is~~ dependent source value should be made '0'.


i.e, the voltage of dependent ^{source} should be made as (0V)

& the current of dependent should be made (0A)

Step 6: The ratio of V_{dc} & I_{dc} is called as R_{Th} (Thevenin resistance)

$$R_{Th} = \frac{V_{dc}}{I_{dc}}$$

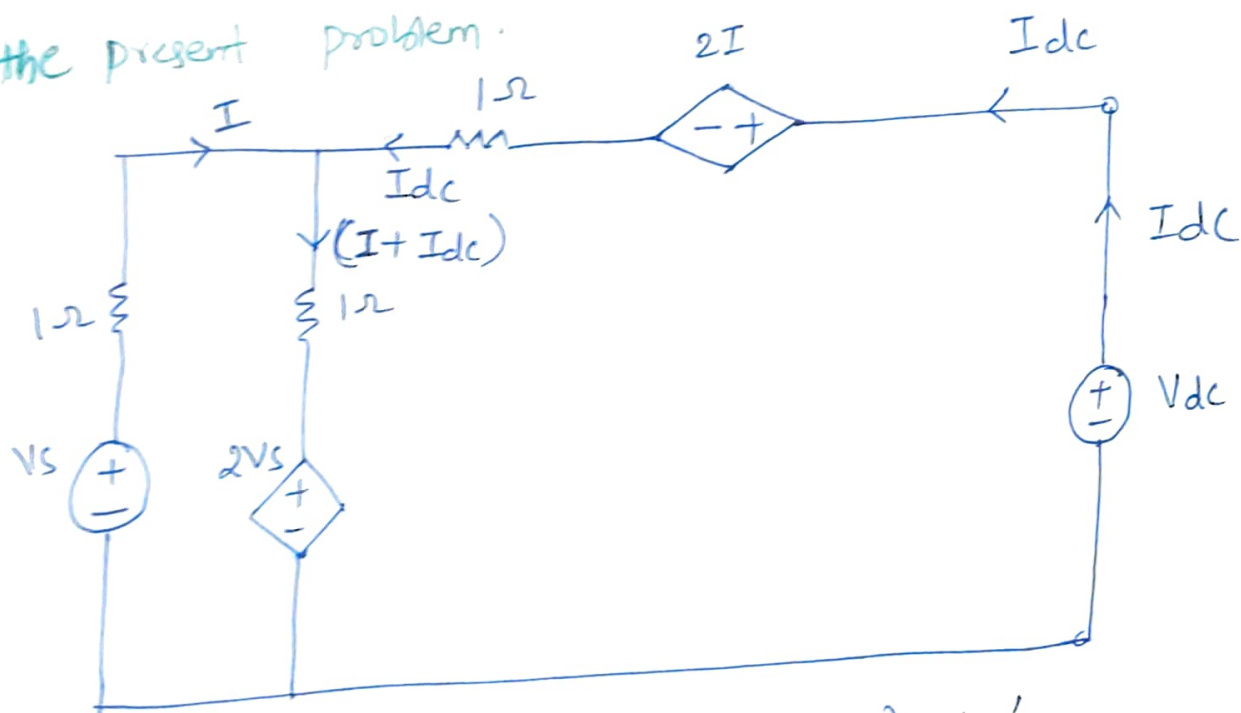Now let us apply the above working rule for ~~this~~ the present problem.



Now make ' V_s ' voltage (independent) '0' i.e, S-C


" $2V_s$ " ~~independent~~ dependent voltage source must ~~not~~ be made S-C because its magnitude depends on the independent voltage source variable V_s

So, ' $2V_s$ ' dependent voltage source is made S-C

→ ' $2I$ ' dependent voltage source must not be made S-C because ' I ' variable does not depend on the independent voltage variable V_s .

→ ' $2I$ ' dependent voltage source is not made S-C

Now

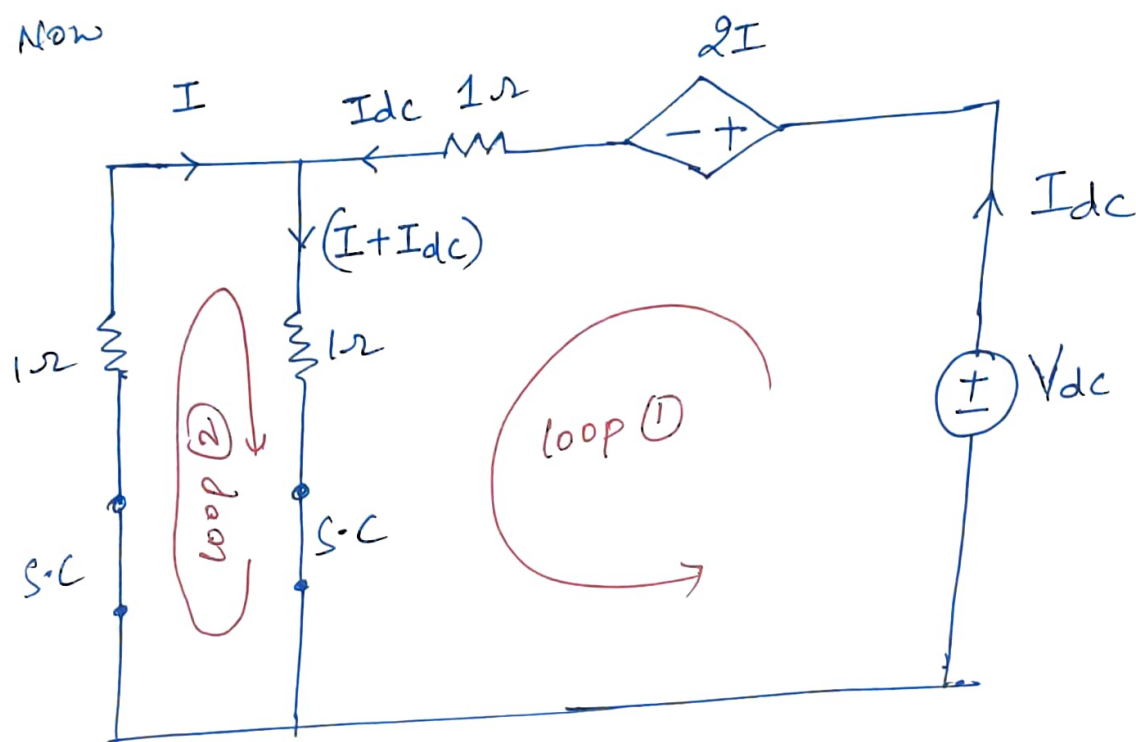

Apply KVL in loop ①

$$V_{dc} - 2I - I_{dc} - (I + I_{dc}) = 0$$

$$V_{dc} - 2I - I_{dc} - I - I_{dc} = 0$$

$$V_{dc} = 3I + 2I_{dc} \longrightarrow \text{①}$$

Apply KVL in loop ②

$$-I - (I + I_{dc}) = 0$$

$$-2I - I_{dc} = 0$$

$$I_{dc} = -2I$$

$$I = -\frac{I_{dc}}{2} \rightarrow (2)$$


put (2) in (1)

$$V_{dc} = 3\left[-\frac{I_{dc}}{2}\right] + 2I_{dc} = \frac{-3I_{dc} + 4I_{dc}}{2}$$

$$V_{dc} = \frac{I_{dc}}{2}$$

$$\boxed{\frac{V_{dc}}{I_{dc}} = R_{Th} = \frac{1}{2} \Omega}$$

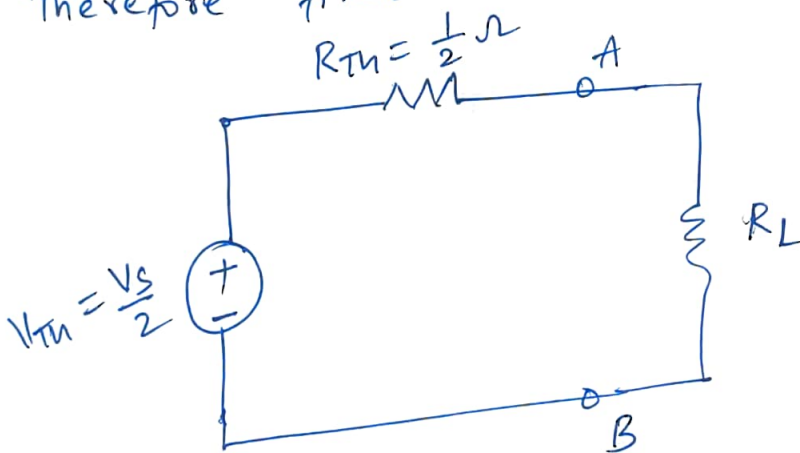Therefore final thevenin equivalent is as follows




Lecture - 4:

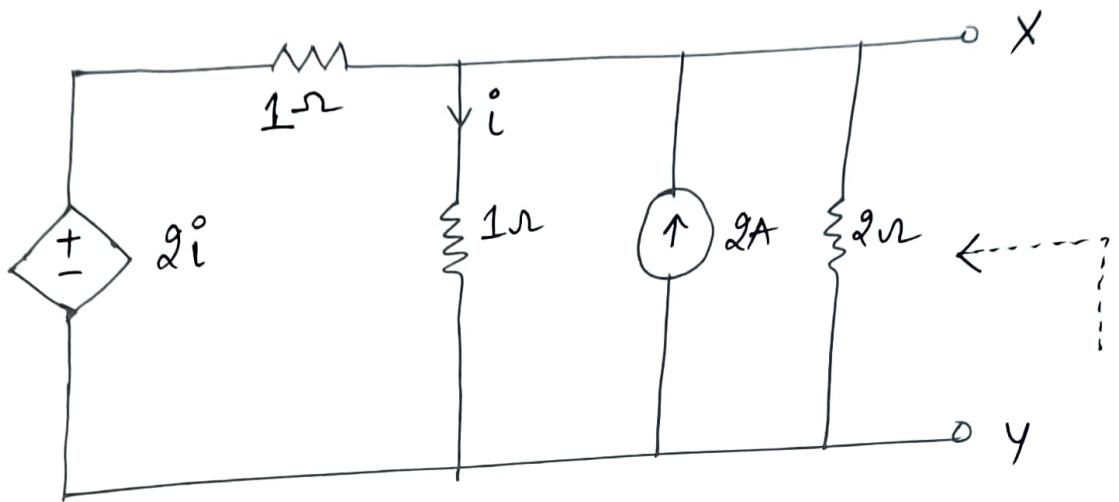Questions Based On Thevenin's Theorem (1)


Q)
GATE
2007

For the ckt shown in figure the thevenin voltage and resistance looking into X-Y are



- A) $\frac{4}{3}V, 2\Omega$ B) $4V, \frac{2}{3}\Omega$ C) $\frac{4}{3}V, \frac{2}{3}\Omega$ d) $4V, 2\Omega$

Soln: To find V_{th} :

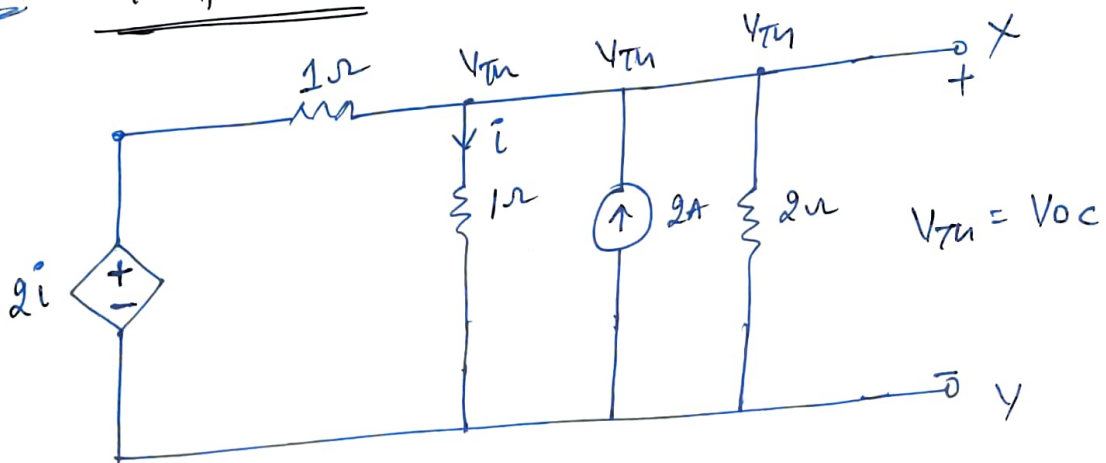

Applying ~~KCL~~ Nodal analysis at V_{th} .

$$\frac{V_{th} - 2i}{1} + \frac{V_{th}}{1} - 2 + \frac{V_{th}}{2} = 0$$

$$\frac{5}{2} V_{th} = 2i + 2$$

$$5V_{th} = 4i + 4 \quad \text{--- (1)}$$

$$V_{Th} = i \times 1 = i \quad \text{--- (2)}$$

put (2) in (1).


$$5V_{Th} = 4V_{Th} + 4$$

$$V_{Th} = 4 \text{ volts}$$

To find R_{Th} :

2A independent current source should be O.C

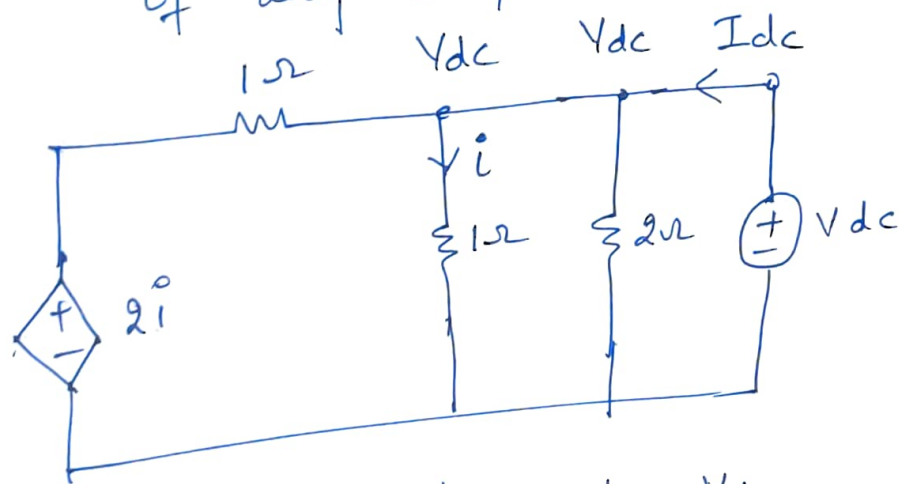2i should be dependent voltage source should not be removed because 'i' is independent of any independent source.



Apply Nodal analysis at V_{dc} .

$$\left(\frac{V_{dc} - 2i}{1} \right) + \frac{V_{dc}}{1} + \frac{V_{dc}}{2} - I_{dc} = 0$$

$$\frac{5}{2}V_{dc} - 2i = I_{dc}$$

$$5V_{dc} = 2I_{dc} + 4i \quad \text{--- (1)}$$

$$V_{dc} = i \quad \text{--- (2)}$$

put (2) in (1)


$$5V_{dc} = 2I_{dc} + 4V_{dc}$$

$$V_{dc} = 2I_{dc}$$

$$R_{Th} = \frac{V_{dc}}{I_{dc}} = 2\Omega$$

Option (D)
is correct.


Thevenin equivalent:

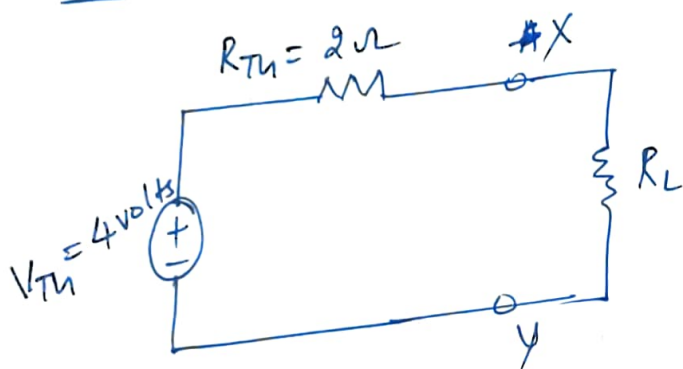

Q) For the ckt shown in fig, Thevenin's voltage & Thevenin's equivalent resistance at terminal a-b is

GATE

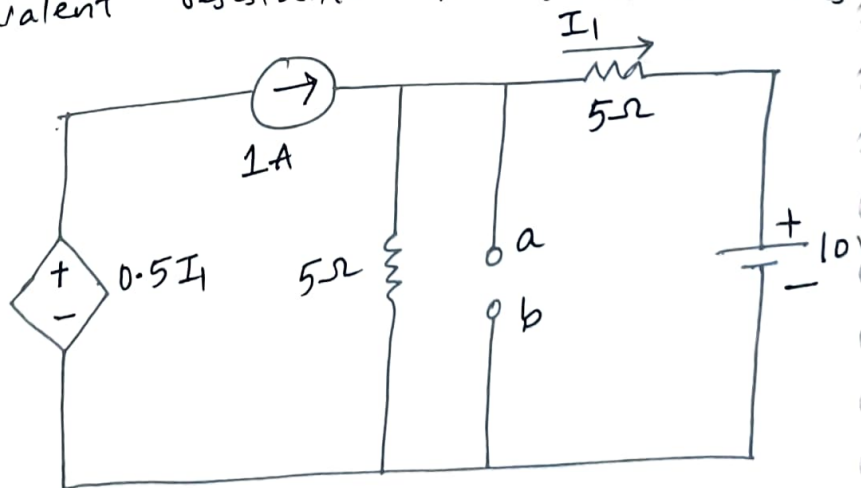- A) 5V & 2Ω
- B) 7.5V & 2.5Ω
- C) 4V & 2Ω
- D) 3V & 2.5Ω



Soln: To find V_{Th} :

Consider the fig given below


Apply KCL at V_{th}

$$\frac{V_{Th}}{5} - 1 + \frac{V_{Th} - 10}{5} = 0$$

$$2V_{Th} - 10 = 5$$

$$2V_{TH} = 15$$

$$V_{TH} = 7.5 \text{ volts}$$

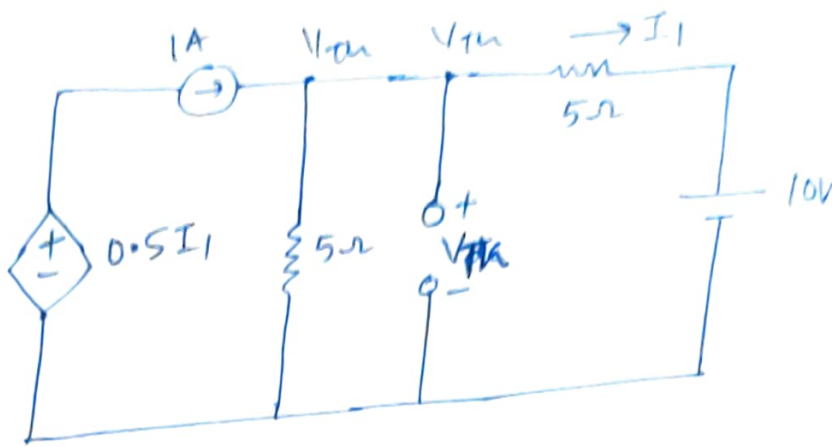



To find R_{Th} :


To find R_{Th} -

~~Open~~ Here we have both dependent & independent source. So, we have to consider V_{dc} & I_{dc} flow a & b terminal & let I_{dc} current ~~flow~~ flow from V_{dc} .

For the $10V$ source

from V_{dc} .

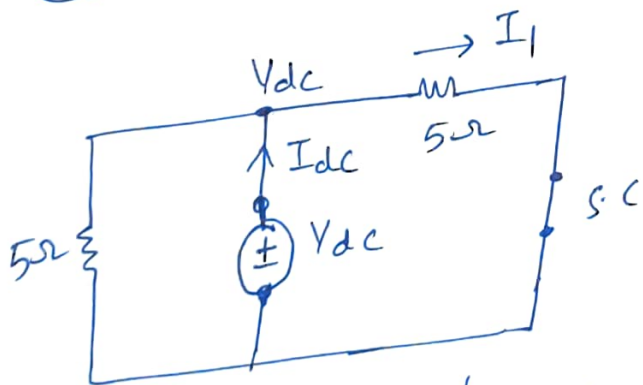(i) Open  & (ii) ~~open~~ S.C the  source



Apply nodal at V_{DC}


$$\frac{V_{dc}}{5} - I_{dc} + \frac{V_d}{5} = 0$$

$$2V_{dc} = 5 I_{dc}$$

$$\frac{V_{dc}}{I_{dc}} = R_{Th} = 2.5 \Omega$$

$$\therefore R_{Th} = 2.5 \Omega$$

Equivalent Thevenin :

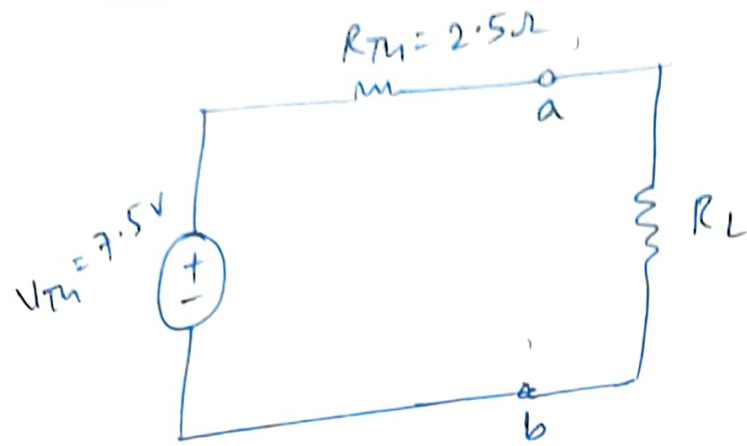


\therefore Option (B) is correct.

Lecture - 5 :

Questions Based on Thevenin's Theorem (2)

Q1) Thevenin's resistance across the terminals A and B is

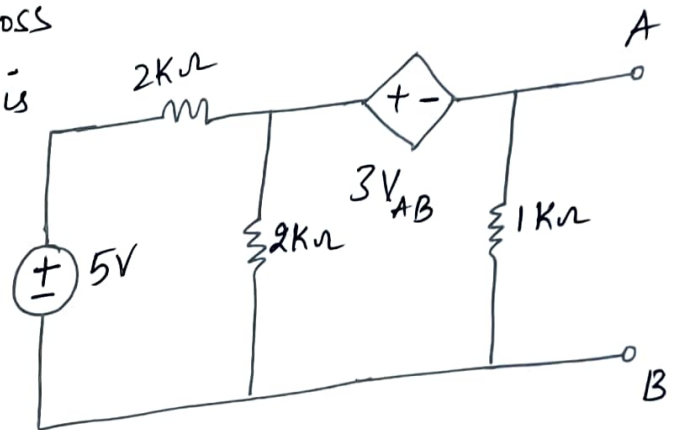- A) $0.5K\Omega$ B) $0.2K\Omega$
C) $1K\Omega$ D) $0.11K\Omega$



Q2) The thevenin voltage across the terminals A & B is

- A) $1.25V$ B) $0.25V$
C) $1V$ D) $0.5V$

Soln To find V_{Th} :


Consider the fig as follows

$$\frac{V_a - 5}{2K} + \frac{V_a}{2K} + \frac{V_{Th}}{1K} = 0$$

$$V_a - 5 + V_a + 2V_{Th} = 0$$

$$2V_a + 2V_{Th} = 5$$

$$V_a + V_{Th} = 2.5 \rightarrow (1)$$

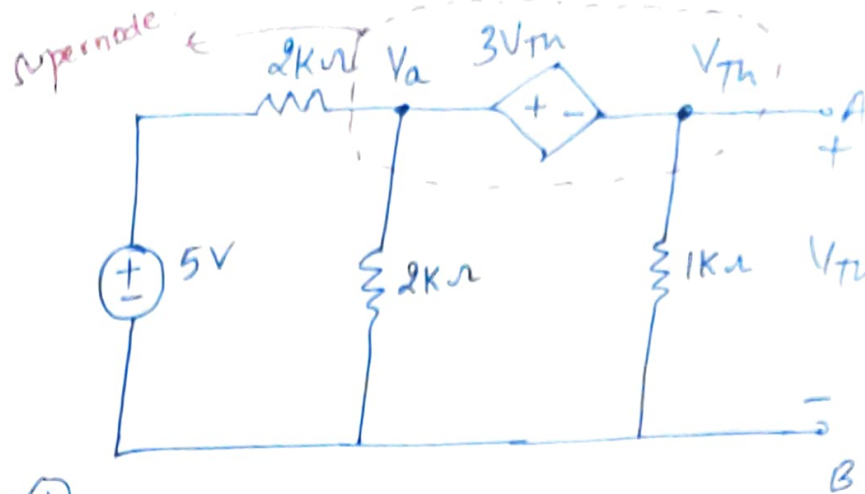

Now, KVL at Supernode

$$V_a - 3V_{Th} + V_{Th} = 0$$

$$V_a = 4V_{Th} \rightarrow (2)$$

put (2) in (1)

$$5V_{Th} = 2.5$$

$$V_{Th} = \frac{2.5}{5} = \frac{1}{2} = 0.5 \text{ volts}$$

$$\therefore V_{Th} = 0.5 \text{ volts}$$


To find R_{Th} :

→ clearly $\textcircled{+} 5V \textcircled{-}$ becomes S.C

→ Apply $\textcircled{+} V_{dc} \textcircled{-}$ b/w 'A & B' and allow I_{dc} current to flow from V_{dc} .

→ The eq. n/w will be modified as follows

Applying supernode analysis.

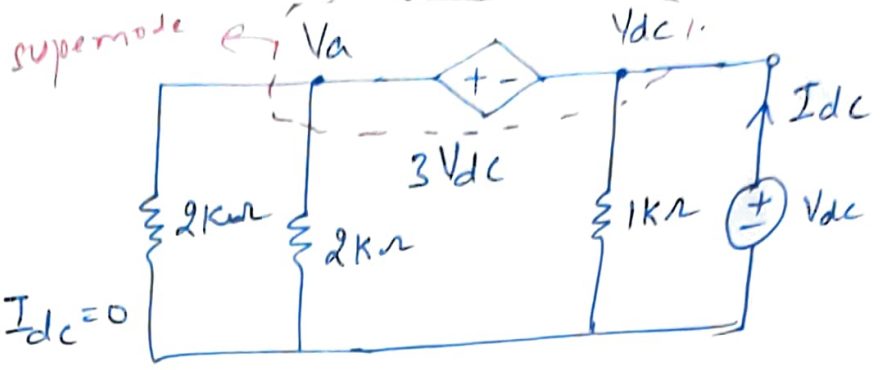

$$\frac{V_a}{2k} + \frac{V_a}{2k} + \frac{V_{dc}}{1k} - I_{dc} = 0$$

$$2V_a + 2V_{dc} = (2k) \times I_{dc}$$

$$V_a + V_{dc} = (1k \times I_{dc}) \rightarrow (1)$$

Now $V_a - 3V_{dc} - V_{dc} = 0$

$$V_a = 4V_{dc} \rightarrow (2)$$

put (2) in (1)

$$4V_{dc} + V_{dc} = (1k \times I_{dc})$$

$$5V_{dc} = 1k \times I_{dc}$$

$$\frac{V_{dc}}{I_{dc}} = \frac{1}{5} k\Omega = R_{Th} = 0.2k\Omega$$

$$\therefore R_{Th} = 0.2k\Omega$$

Thevenin Equivalent:

