

# CHAPTER - 7

## RESONANCE

### Lecture - 01

#### SERIES RLC RESONANCE CIRCUIT :


#### RESONANCE :

- Resonance describes the circuit condition in which (i) Inductive & capacitive features neutralize with each other.
- (ii) Powerfactor of circuit will be unity.
- (iii) Impedance of circuit will become resistive in nature.
- (iv) Input voltage and input current will be in phase.
- Resonance describes the energy transfer between the capacitor and inductor at a constant freq rate.
- The freq rate at which energy transfer will happen between capacitor & inductor is called as "resonance frequency" (OR) "frequency of oscillation".

## 1. Series RLC Network

$$V = V_R + j(V_L - V_C) \rightarrow (1)$$

$$Z = R + j(X_L - X_C) \rightarrow (2)$$

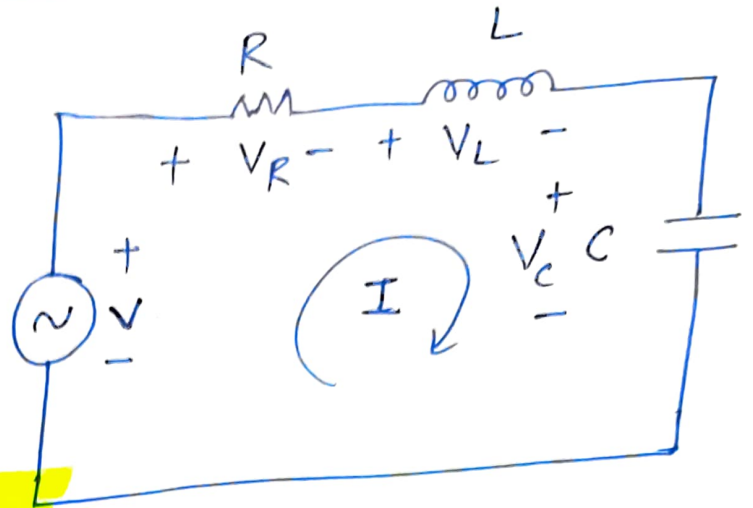

Condition of Resonance:

$$\text{Im}[V] = 0$$

$$(OR) \text{Im}(Z) = 0$$

$$V_L - V_C = 0$$

$$X_L - X_C = 0$$

$$V_L = V_C$$

$$X_L = X_C$$

$$I X_L = I X_C$$

$$X_L = X_C$$

For the case of resonance  $\Rightarrow Z = R$

Now, we have

$$X_L = X_C$$


$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC}$$


$\Rightarrow$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$
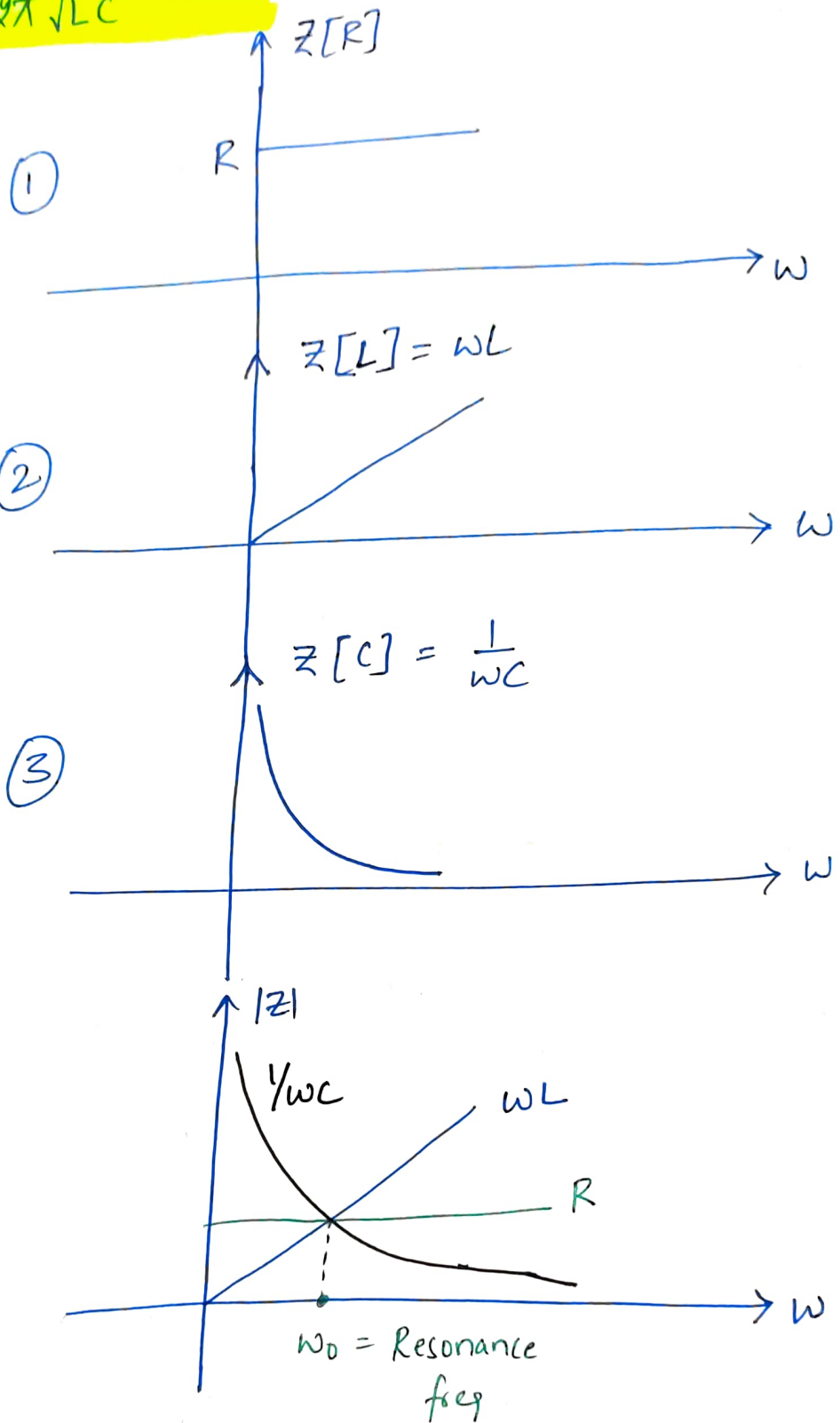
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$



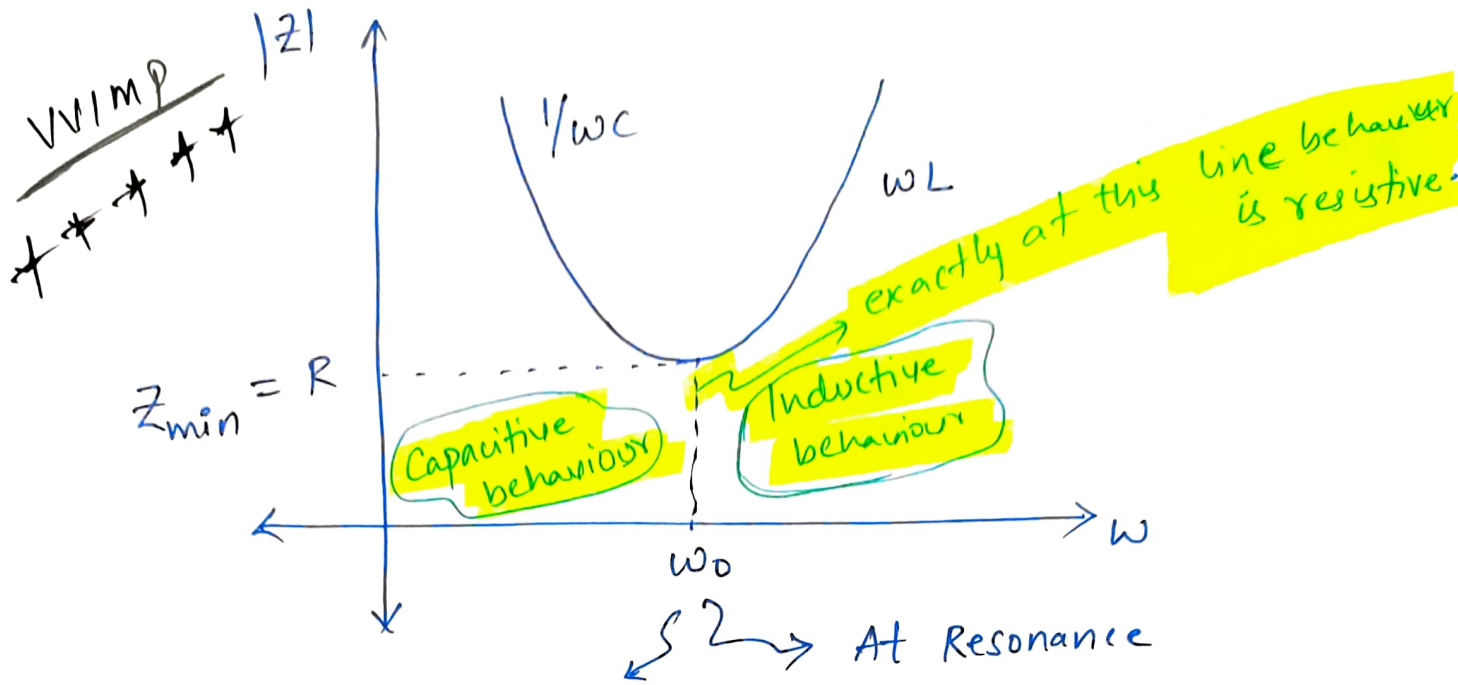If we combine (1), (2) & (3). The graph obtained is drawn as follows :




Here the  
behaviour is resistive  
in nature.

VVIMP

$\omega$	$R/L/C$	Power Factor
$\omega < \omega_0$	Capacitive (C)	Leading
$\omega > \omega_0$	Inductive (L)	Lagging
$\omega = \omega_0$	Resistive (R)	Unity Power factor (UPF)

$$I = \frac{V}{Z} = \frac{V \angle 0^\circ}{R + j(\omega L - 1/\omega C)}$$

$$|I| = \frac{V}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

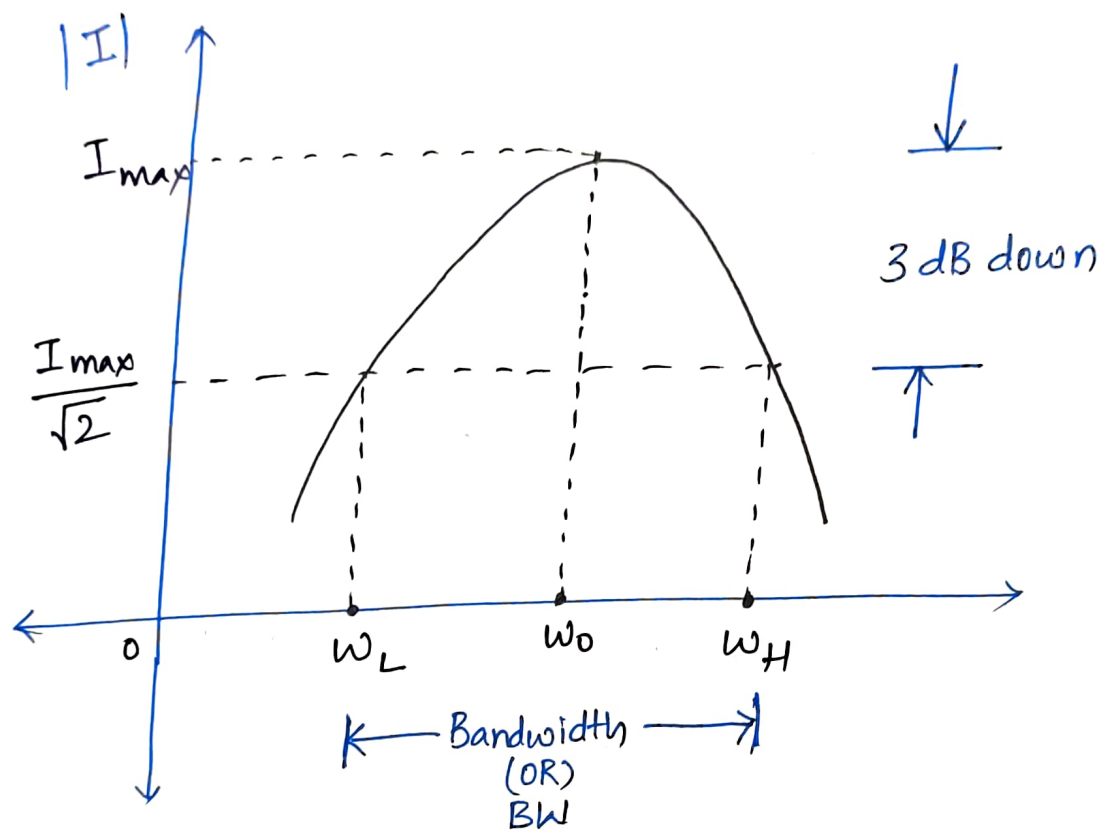

$\omega_L$  : lower 3dB freq ;  $BW = \text{Bandwidth}$ .

$\omega_H$  : upper (or) higher 3dB freq. ;

At  $\omega = \omega_0 \Rightarrow$  (i)  $Z_{min} = R$

(ii)  $I_{max} = \frac{V_{min}}{R}$ .

Series RLC resonance ckt is also called as acceptor ckt because it accepts maximum current at resonance



$$\text{Bandwidth} = \omega_H - \omega_L$$

Now

$$x \xrightarrow{\text{dB}} 20 \log_{10} x$$

$$\frac{1}{\sqrt{2}} \xrightarrow{\text{dB}} 20 \log_{10} \frac{1}{\sqrt{2}} = -3.010 \text{ dB}$$

If the  $I_{\text{max}}$  decreases to  $\frac{I_{\text{max}}}{\sqrt{2}}$  (or)  $0.707 I_{\text{max}}$  then there will be 3dB down (i.e. -3dB) from the max current  $I_{\text{max}}$  (in dB).

Q) Here the ckt is in series, but how the current changes in series?

Ans: The current changes w.r.t angular frequency " $\omega$ ". If ' $\omega$ ' changes the impedance ( $Z$ ) changes. If impedance ( $Z$ ) changes then the current changes. So, this is the answer.

Calculation of 3dB frequency :

3-dB frequency :

The frequency at which current response will be 70.7% or  $\frac{1}{\sqrt{2}}$  times of its max current value, is called as 3dB frequency

$$|I| = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

At  $I = I_{\max}$  ;  $P_0 = I_{\max}^2 R$

At  $I = \frac{I_{\max}}{\sqrt{2}}$  ;  $P_0' = \left(\frac{I_{\max}}{\sqrt{2}}\right)^2 R = \frac{I_{\max}^2 R}{2}$

At  $I = 0.707 I_{\max}$  ;  $P_0' = \frac{P_0}{2}$

→ If the max current  $I_{\max}$  changes from  $I_{\max}$  to  $\frac{I_{\max}}{\sqrt{2}}$  then the maximum power changes from  $P_0$  to  $\frac{P_0}{2}$  (i.e. it will be halved).

→ That is why we call the  
 $\omega_L$  : lower half power frequency  
 $\omega_H$  : higher half power frequency

$$|I| = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\frac{I_{\max}}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + \left(\omega_{3\text{-dB}} L - \frac{1}{\omega_{3\text{-dB}} C}\right)^2}}$$

$$I_{\max} = \frac{V}{R}$$

$$\frac{V}{R\sqrt{2}} = \frac{V}{\sqrt{R^2 + \left(\omega_{3-dB}L - \frac{1}{\omega_{3-dB}C}\right)^2}}$$

$$R^2 + \left(\omega_{3-dB}L - \frac{1}{\omega_{3-dB}C}\right)^2 = 2R^2$$

$$\left(\omega_{3-dB}L - \frac{1}{\omega_{3-dB}C}\right)^2 = \pm R \rightarrow \textcircled{I}$$


$$\omega_{3-dB}L - \frac{1}{\omega_{3-dB}C} = R \quad (\text{OR}) \quad \omega_{3-dB}L - \frac{1}{\omega_{3-dB}C} = -R$$

$$\left(\omega_H L - \frac{1}{\omega_H C}\right) = R \rightarrow \textcircled{1}$$

why?

$$\left(\omega_L L - \frac{1}{\omega_L C}\right) = -R \rightarrow \textcircled{2}$$

why?

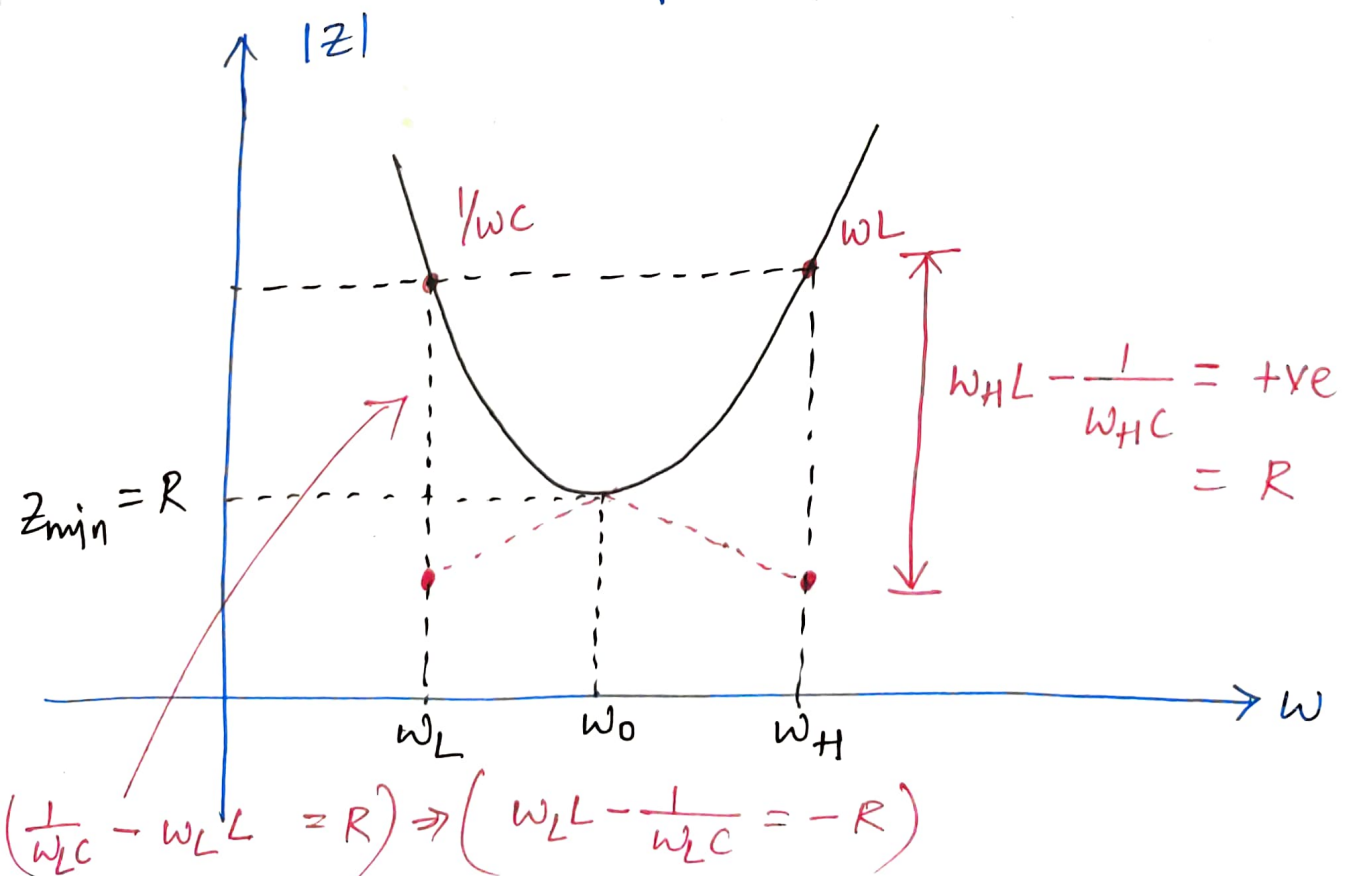



Now from ① + ②

~~$\omega_H$~~  from ①

$$\omega_H^2 LC - 1 = \omega_H RC$$

$$\omega_H^2 LC - \omega_H RC - 1 = 0$$

$$\omega_H^2 - \omega_H \frac{R}{L} - \frac{1}{LC} = 0$$

$$\omega_H = \frac{\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}}}{2}$$

$$\omega_H = \frac{\frac{R}{L} + \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}}}{2}$$

$$\omega_H = \left( \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right) \text{ rad/sec}$$

Similarly

$$\omega_L = \left( -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right) \text{ rad/sec}$$

$$\text{Bandwidth} = BW = \omega_H - \omega_L$$

$$\therefore BW = \frac{R}{2L} - \left(-\frac{R}{2L}\right) = \frac{R}{L}$$

~~$$\therefore \text{Bandwidth} = \frac{R}{L}$$~~

$$\text{Bandwidth} = \frac{R}{L} \text{ rad/sec} = \frac{R}{2\pi L} \text{ Hz}$$

$$\text{Bandwidth} = \text{function}(R, L)$$

$$\text{Bandwidth} \neq \text{function}(C)$$

VVIMP

$$\text{Now } \omega_H \omega_L = \left( \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right) \left( -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right)$$

$$\omega_H \omega_L = -\left(\frac{R}{2L}\right)^2 + \left[\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}\right]$$

$$\omega_H \omega_L = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$\omega_0^2 = \omega_H \omega_L = \frac{1}{LC}$$

$$\omega_H = \frac{BW}{2} + \sqrt{\left(\frac{BW}{2}\right)^2 + \omega_0^2}$$

$$\omega_L = -\frac{BW}{2} + \sqrt{\left(\frac{BW}{2}\right)^2 + \omega_0^2}$$

If  $\omega_0 \gg BW$

$$\rightarrow \omega_H \approx \frac{BW}{2} + \omega_0$$

$$\rightarrow \omega_L \approx -\frac{BW}{2} + \omega_0$$


SATYA

REPARATION


IS IN THE FINAL  
PHASE ...

GOOD !!

AWESOME

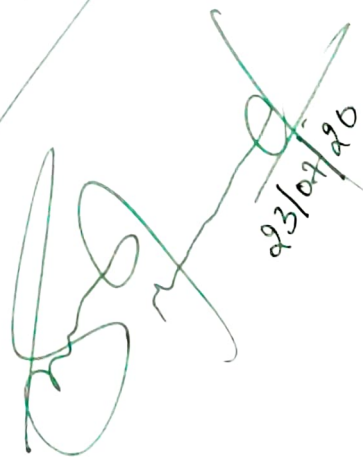  
23/07/20

$\omega$	$\omega L - \frac{1}{\omega C}$	$ Z  = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$	$\angle Z = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$	$I = \frac{V}{Z}$	Power Factor
$\omega = \omega_H$ ( $\omega > \omega_0$ )	$\omega_H L - \frac{1}{\omega_H C}$	$ Z  = \sqrt{R^2 + R^2} = \sqrt{2}R$	$\angle Z_H = \tan^{-1}(1) = 45^\circ$	$I_H = \frac{V}{\sqrt{2}R} \angle -45^\circ$	$\cos 45^\circ = 0.707$ lagging
$\omega = \omega_L$ ( $\omega < \omega_0$ )	$\omega_L L - \frac{1}{\omega_L C}$	$ Z_L  = \sqrt{2}R$	$\angle Z_L = -45^\circ$	$I_L = \frac{V}{\sqrt{2}R} \angle 45^\circ$	$\cos 45^\circ = 0.707$ leading
$\omega = \omega_0$	$\omega_0 L - \frac{1}{\omega_0 C} = 0$	$Z_{\min} = R$	$\angle Z_0 = 0^\circ$	$I_0 = \frac{V}{R} \angle 0^\circ$	Unity power factor i.e. PF = 1
Don't Remember this table. Its WIMP. (create it)					

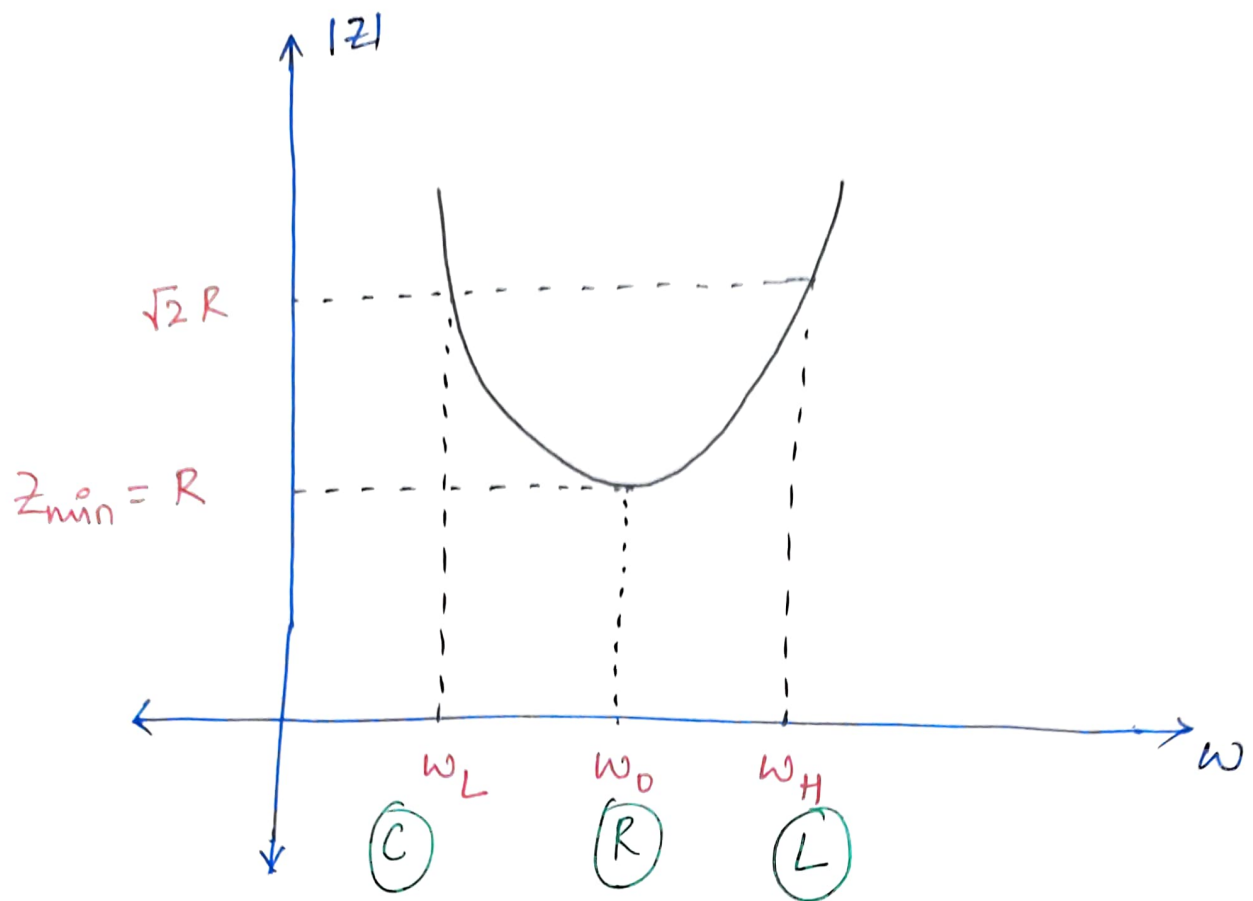

### 3-dB Impedance Phasor Diagram :

