

Date: 16/06/19

CHAPTER - 2

TWO-PORT NETWORKS THEOREMS

Lecture - 1

Introduction of Two Port Network:

One Port n/w:

A n/w which has only one port (i.e, i/p port or output port) is called as one port network.


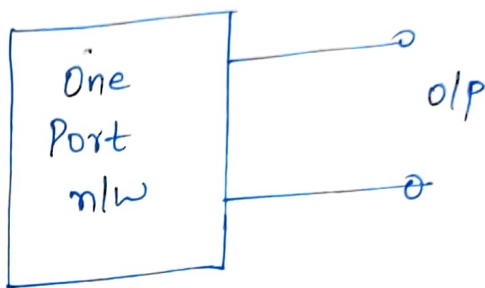
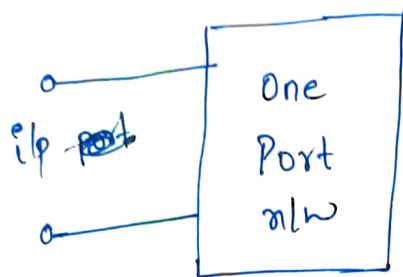


fig: One port n/w.


Eg: Generator, Motor etc

Two Port n/w:

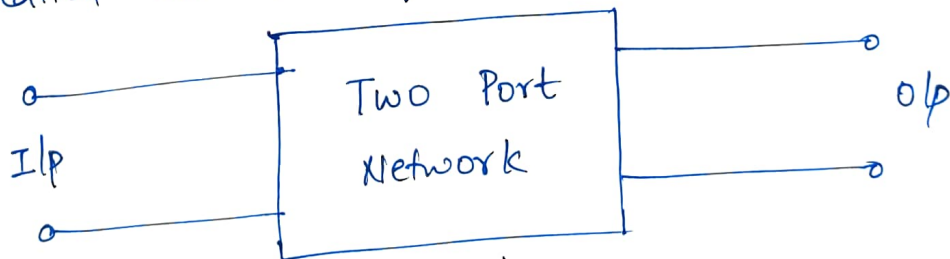
A n/w which has both 2 ports (input & output ports) is called as two port network.




Symbolic Notation:

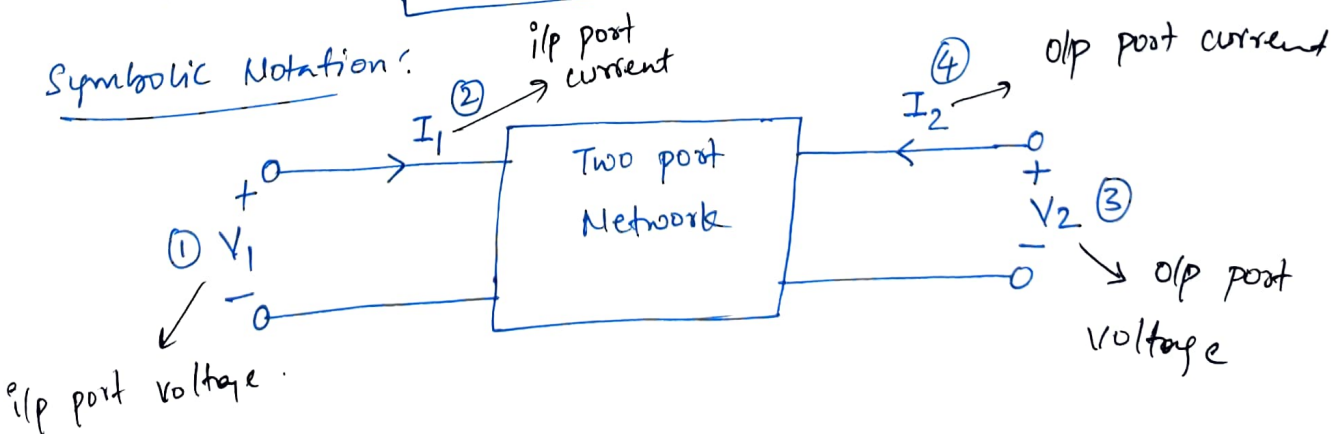

Eg: ① Transformer

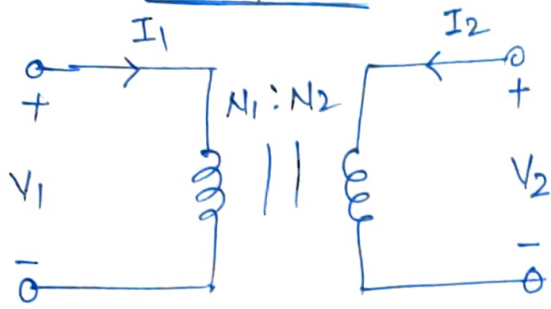


② Transistor:

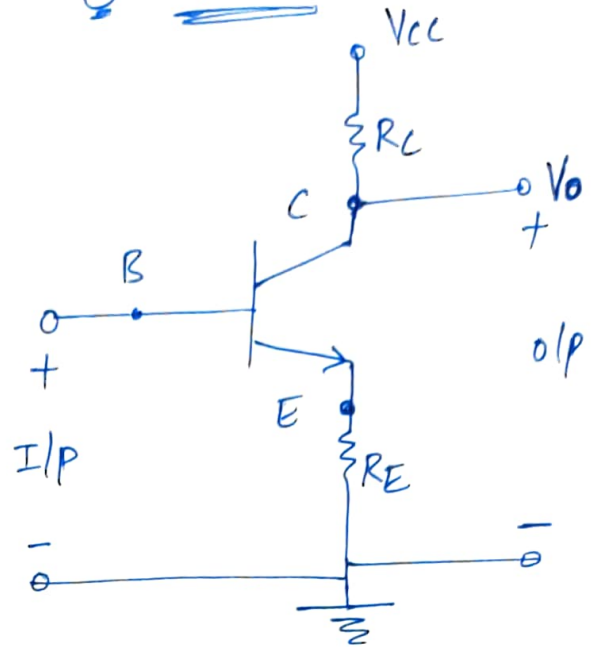

Important Concept:

Consider

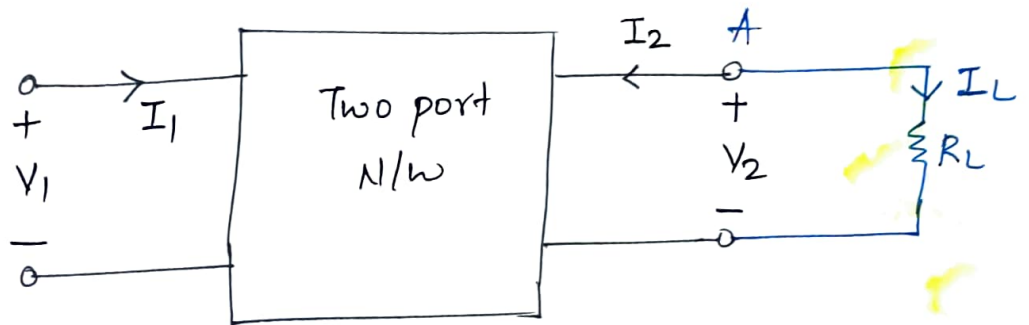

o/p voltage $V_2 = I_L R_L$

By KCL at A $\Rightarrow I_L = -I_2$

So. o/p voltage $V_2 = -I_2 R_L$

~~VVIMP~~

VVIMP
concept

I_L = load current.

R_L = load resistance

I_2 = o/p port current

V_2 = o/p voltage.

Possible combinations of Two Port n/w:


We have 4 variables V_1, I_1, V_2, I_2

We have to select two variables out of 4.
(one i/p & other o/p)

→ So possible combinations of Two port n/ws = ${}^4C_2 = 6$.

The possible two port parameters are:

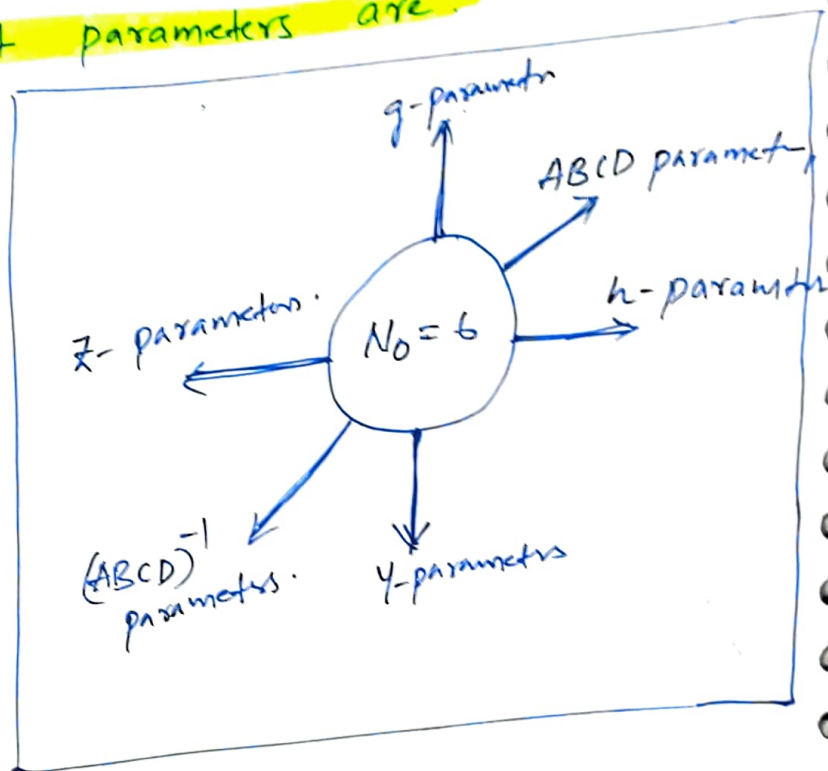1. Z -parameters
2. Y -parameters
3. h -parameters
4. g -parameters
5. ABCD-parameters
6. Inverse ABCD $(ABCD)^{-1}$ parameters



LECTURE - 2

Introduction to Z-Parameters:

Z-Parameters (or) Impedance Parameters:

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow \textcircled{1} \Rightarrow \text{i/p KVL eq'n}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow \textcircled{2} \Rightarrow \text{o/p KVL eq'n}$$

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$

Here Independent Variables = I_1, I_2

Dependent Variables = V_1, V_2 .

Conditions for Existence of Z-parameters:

1. I_1 & I_2 must be independent to each other.

i.e., if $I_1 = f(\text{only } I_2)$ (or) $I_2 = f(\text{only } I_1)$

In this case Z-parameters does not exist.

Z-parameter model: (or) Impedance Model:

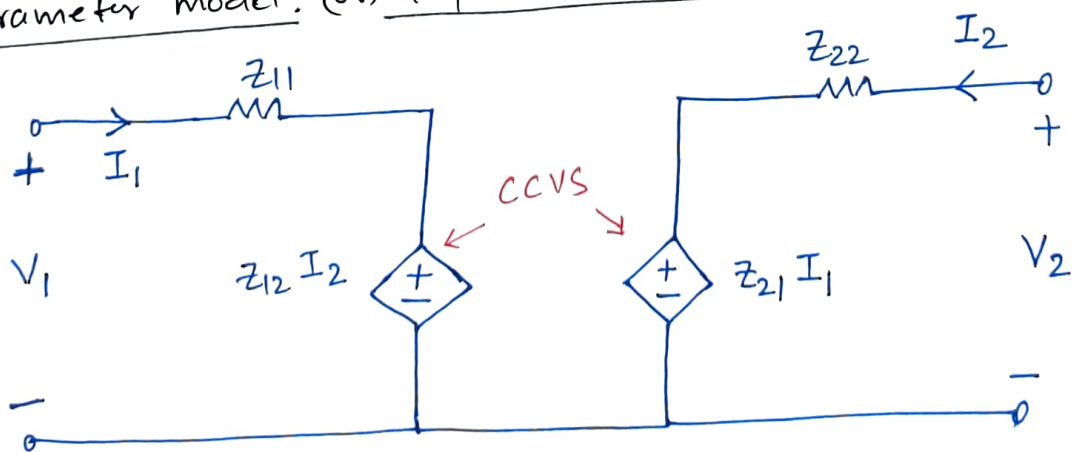


fig: Impedance Model.

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \text{Driving point i/p impedance when o/p is open ckt (O.C)}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \text{Transfer i/p impedance when i/p is open ckt (O.C)}$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \text{Transfer o/p impedance when o/p is open ckt (O.C)}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \text{Driving point o/p impedance when i/p is open ckt (O.C)}$$

Note (i) All these impedances are conditional impedances. Because here we are finding impedance by opening either i/p or o/p.


→ (ii) So, we can conclude that Z-parameter model is open ckt parameter model.

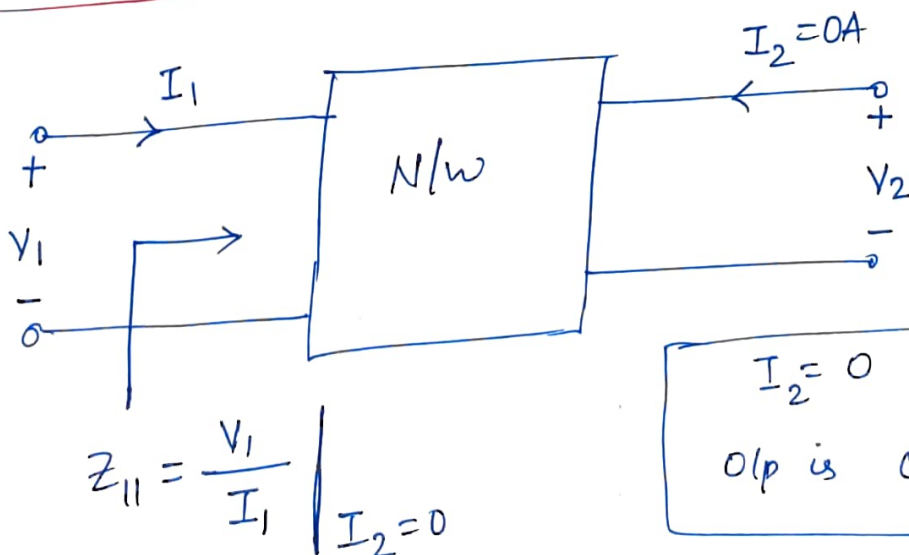Z_{11} structure (or) Driving pt i/p impedance structure:



$I_2 = 0$ because
o/p is O.C

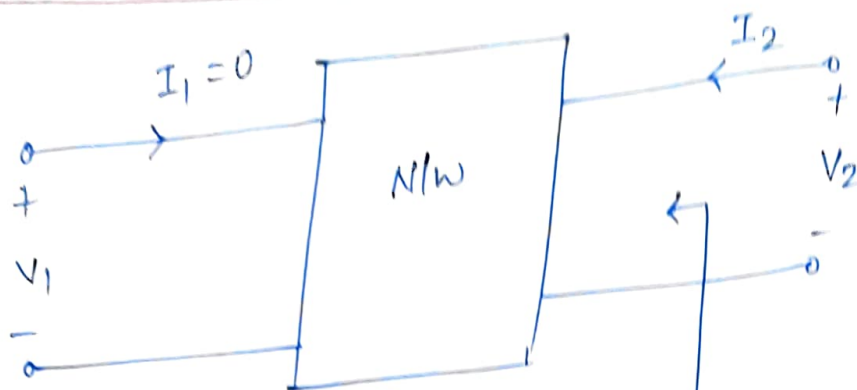Z_{22} structure (or) Driving pt o/p impedance structure:



$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1 = 0}$$

Here $I_1 = 0$
because i/p is
open ckt O.C


Note: 1) We cannot represent Z_{12} & Z_{21} with \leftarrow or \rightarrow because it is neither on i/p side nor on o/p side. So, we cannot draw structure for Z_{12} & Z_{21} as that of Z_{11} & Z_{22} .

2) $\rightarrow \Rightarrow$ Implies voltage & current at the position of arrow & $Z = \left(\frac{V}{I}\right)$ at position of arrow

Now Consider the following network.

Here $Z_{in} \neq Z_{11}$

Z_{11} is conditional impedance

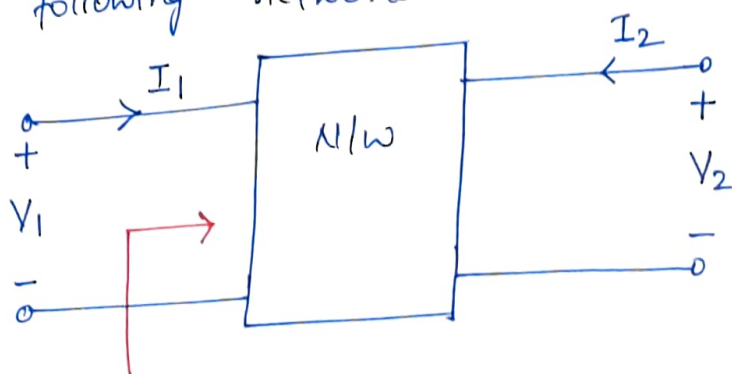

$$Z_{in} = \frac{V_1}{I_1} = \text{Unconditional i/p impedance.}$$

Understand the diff b/w Z_{in} & Z_{11} .

Eg: Input impedance in transformer or transistor is unconditional.

Matrix Representation of Z-parameter Model:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}_{2 \times 1} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}_{2 \times 2} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_{2 \times 1}$$

i.e., $[V] = [Z][I]$

Z-matrix $= [Z]_{2 \times 2} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}_{2 \times 2}$

$\Delta Z = z_{11}z_{22} - z_{12}z_{21} = \text{Determinant of } Z$

Adj $Z = \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix} = \text{Adjoint of } Z$

$[Z^{-1}] = \frac{\text{Adj } Z}{\Delta Z} = \frac{1}{\Delta Z} \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix} = \text{Inverse of } Z$

Example: Find the Z-parameters for following T n/w?


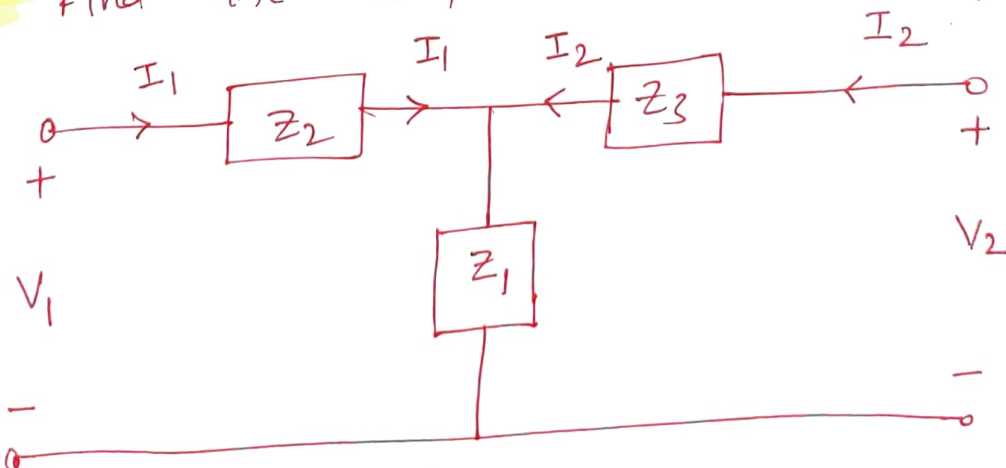


fig T N/w

sol.

Consider

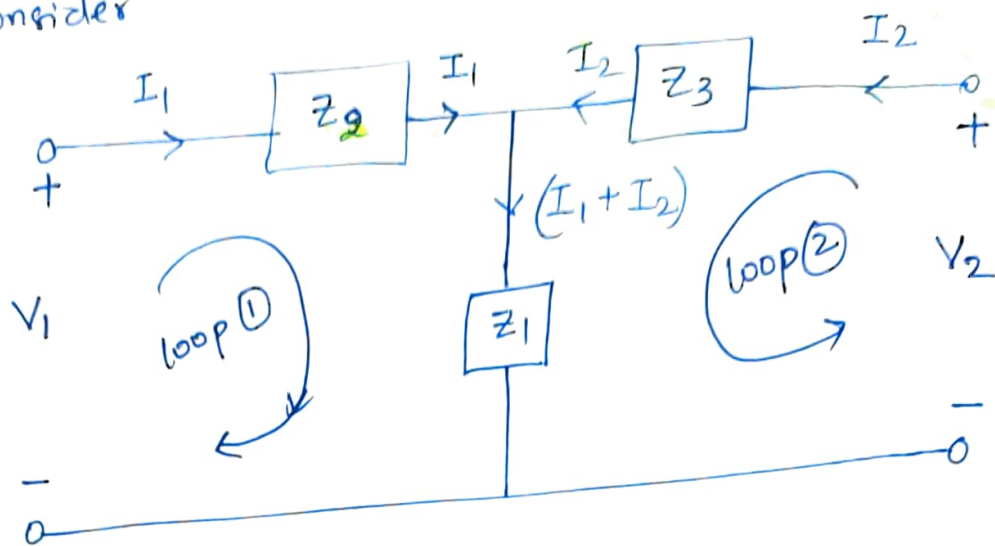

Apply KVL in loop ①

$$V_1 - Z_2 I_1 - (I_1 + I_2) Z_1 = 0$$

$$V_1 - Z_2 I_1 - Z_1 I_1 - Z_1 I_2 = 0$$

$$V_1 = (Z_1 + Z_2) I_1 + (Z_1) I_2 \longrightarrow \textcircled{1}$$

Comparing ① with

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

we get $Z_{11} = Z_1 + Z_2$ & $Z_{12} = Z_1$

Apply KVL for loop ②

$$V_2 - I_2 Z_3 - (I_1 + I_2) Z_1 = 0$$

$$V_2 = I_1 (Z_1) + (Z_1 + Z_3) I_2 \longrightarrow \textcircled{2}$$


Comparing ② with

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$Z_{21} = Z_1$ & $Z_{22} = Z_1 + Z_3$

$$\therefore [Z]_{2 \times 2} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix} \rightarrow \text{Remember the result.}$$

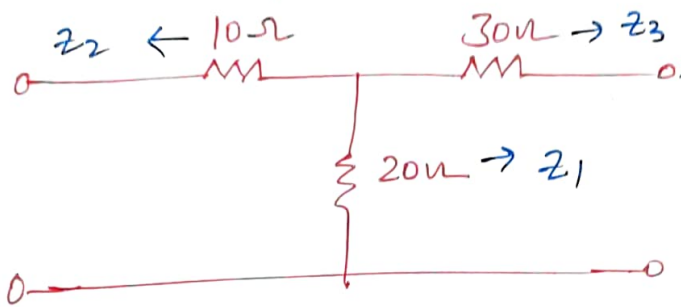Eg: Find the Z-parameters for the given n/w.




Sol By comparing with the standard n/w.



$$[Z]_{2 \times 2} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix}$$

$$\therefore [Z]_{2 \times 2} = \begin{bmatrix} 20 + 10 & 20 \\ 20 & 20 + 30 \end{bmatrix} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}$$

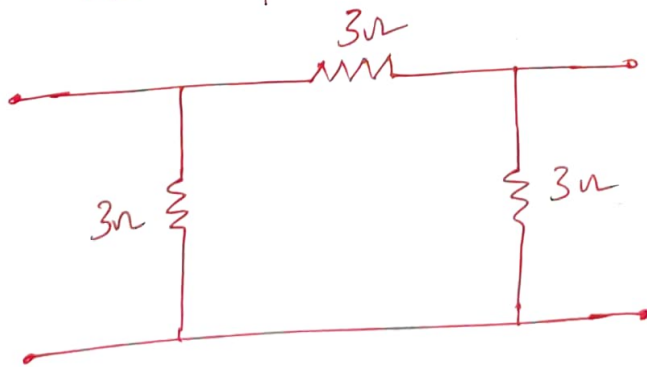
Eg: Find the Z-parameters for the given n/w.



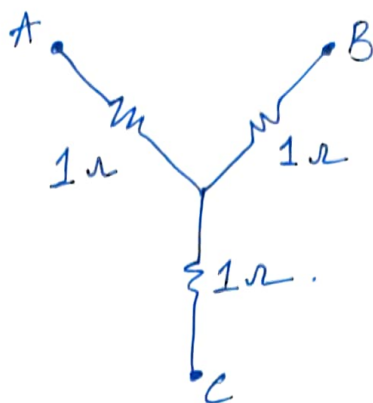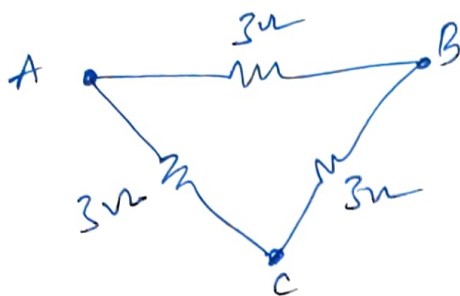Sol. Convert the given delta n/w to ~~the~~ T (or) star n/w.




Now.

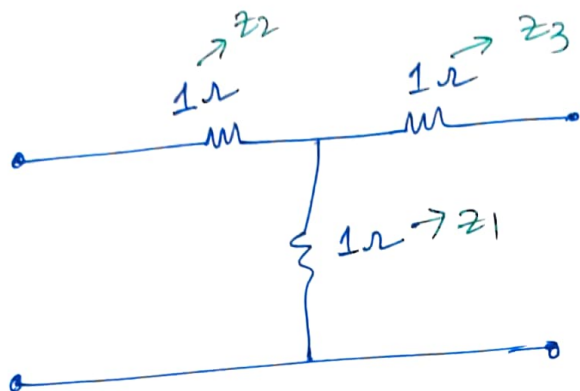


$$[Z]_{2 \times 2} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix} = \begin{bmatrix} 1+1 & 1 \\ 1 & 1+1 \end{bmatrix} = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}$$

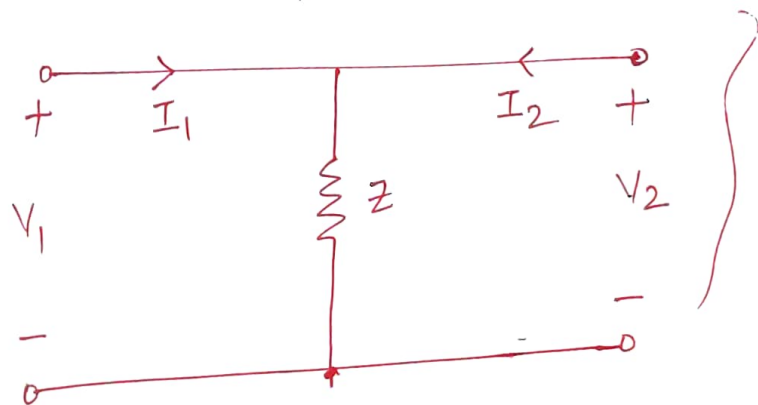Eg: Consider the shunt n/w and find the z -parameters.



→ single shunt element

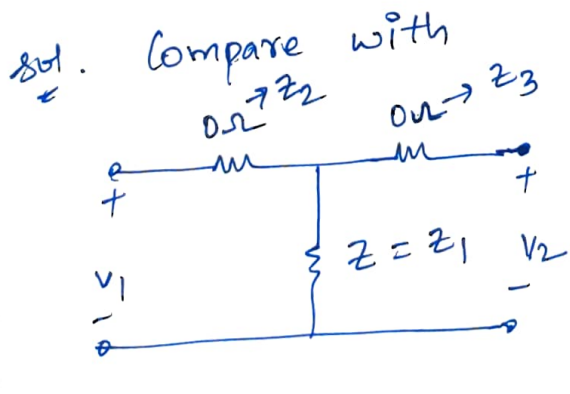

$$[Z] = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix}$$

$$[Z] = \begin{bmatrix} z+0 & z \\ z & z+0 \end{bmatrix} = \begin{bmatrix} z & z \\ z & z \end{bmatrix}$$

Example: Consider the π single series element n/w and find the 2-parameters for the given n/w.


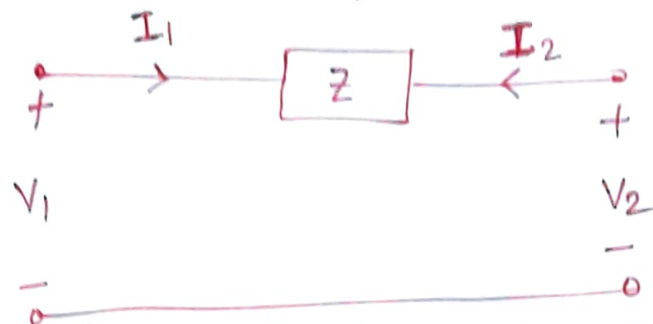


fig: Single Series Element

The given n/w can be transformed as

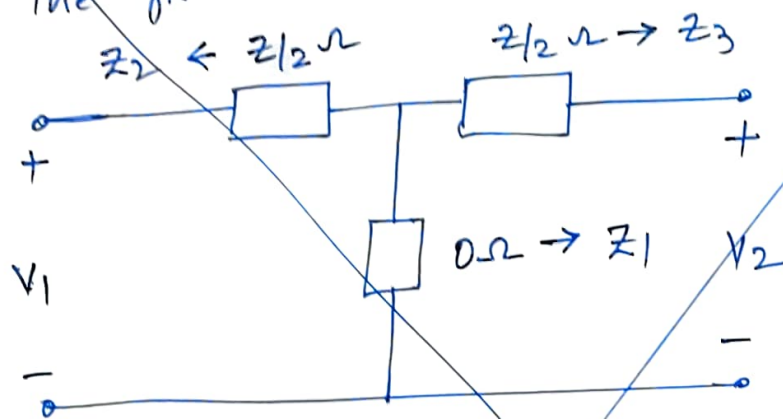

$$[Z]_{2 \times 2} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix} = \begin{bmatrix} 0 + z/2 & 0 \\ 0 & 0 + z/2 \end{bmatrix}$$

$$\therefore [Z]_{2 \times 2} = \begin{bmatrix} z/2 & 0 \\ 0 & z/2 \end{bmatrix}_{2 \times 2}$$

from the above n/w. we can say that

$$I_1 + I_2 = 0$$

$$I_1 = -I_2$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \rightarrow \left(\begin{array}{l} \text{If } I_2 = 0 \\ \text{then } I_1 = 0 \end{array} \right) \quad Z_{11} = \frac{V_1}{0} = \infty$$

$$\boxed{\therefore Z_{11} = \infty}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \Rightarrow Z_{12} = \frac{V_1}{0} = \infty ; \quad \boxed{\therefore Z_{12} = \infty}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Rightarrow Z_{21} = \frac{V_2}{0} = \infty ; \quad \boxed{Z_{21} = \infty}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \Rightarrow Z_{22} = \frac{V_2}{0} = \infty ; \quad \boxed{\therefore Z_{22} = \infty}$$

$$\therefore [Z]_{2 \times 2} = \begin{bmatrix} \infty & \infty \\ \infty & \infty \end{bmatrix}_{2 \times 2}$$


NOTE: For a single series element n/w, Z-parameters do not exist.

→ Here I_1 & I_2 are dependent (ie, $I_2 = -I_1$)

I_2 can be derived from I_1 in this n/w.

→ We know that for a n/w with dependent currents Z-parameters do not exist.

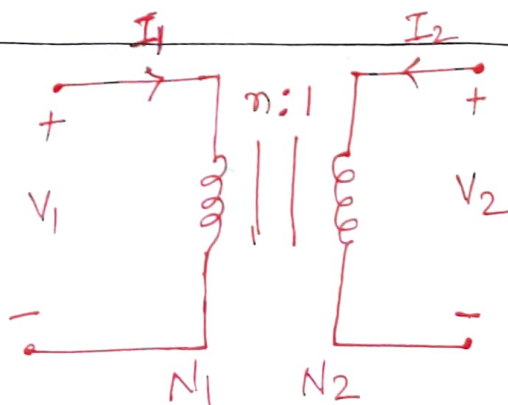Eg: Find the Z-parameters for the ideal transformer as shown in the fig



sol. Here $\frac{V_1}{V_2} = \frac{n}{1} = \frac{N_1}{N_2} \rightarrow (1)$

$-\frac{I_2}{I_1} = \frac{n}{1} = \frac{N_1}{N_2} \rightarrow (2)$

Here clearly $-I_2 = n I_1$


i.e., I_1, I_2 are dependent variables.

So, we can say that 'z' parameters do not exist for the ideal transformer.

Lecture - 3 :


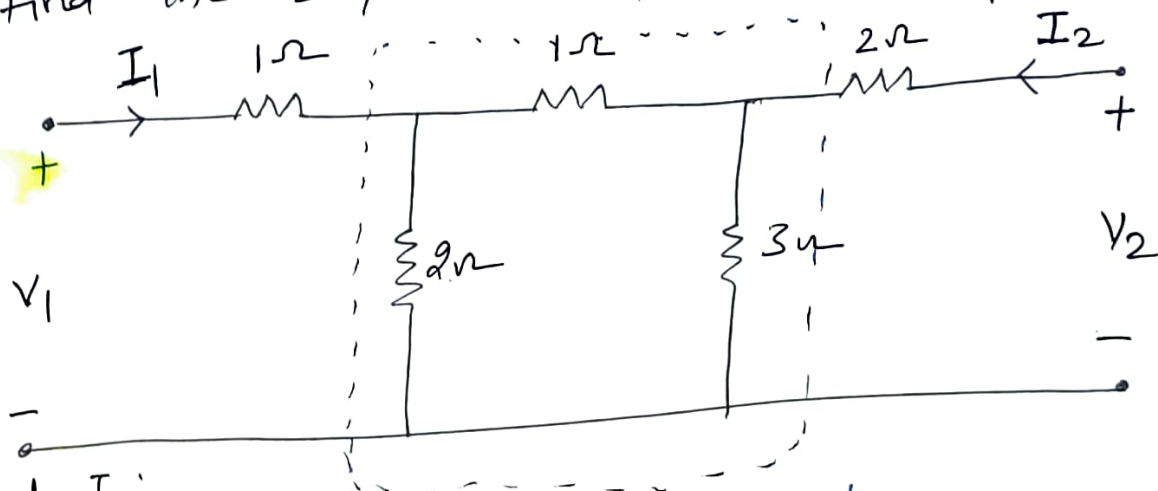
Examples Based On z-Parameters :

Ex 1: Find the z-parameters for the following n/w.




Method - I :

sol. Here we observe the delta n/w.

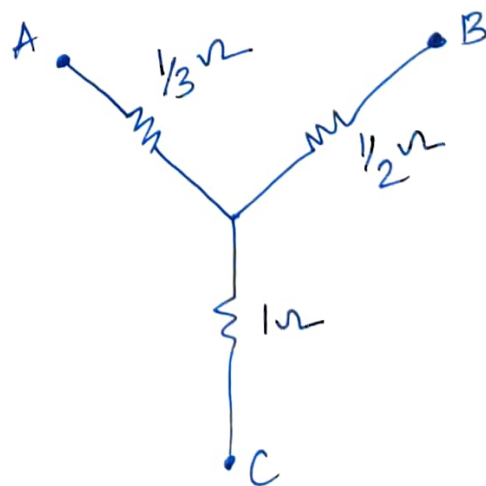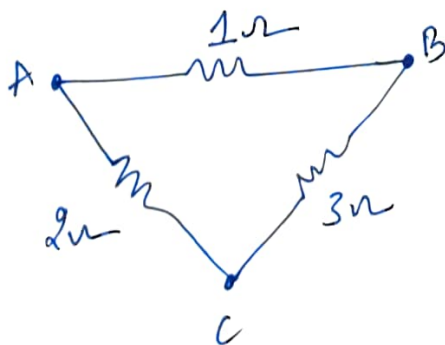

The given n/w is transformed as follow.

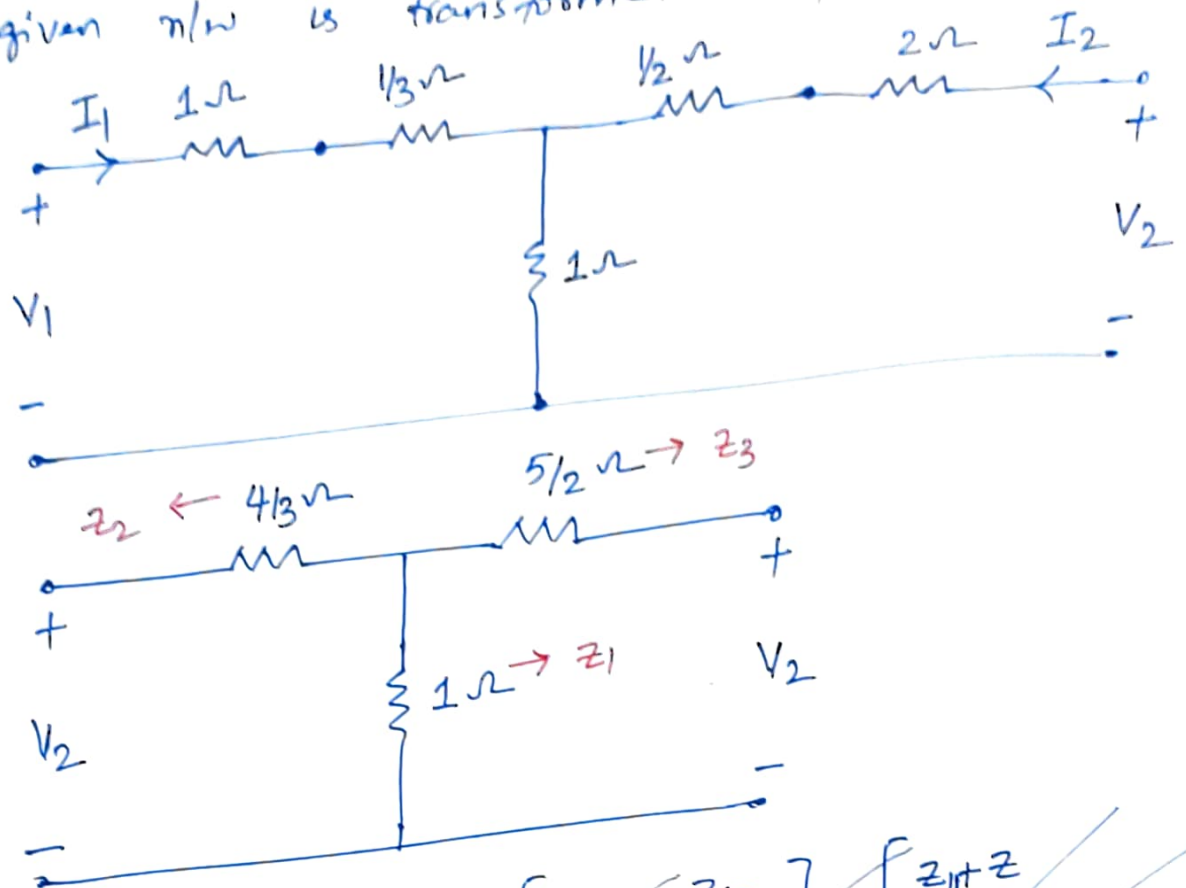

We have $[Z]_{2 \times 2} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix}$

$$[Z]_{2 \times 2} = \begin{bmatrix} z_1 + z_2 & z_1 \\ z_1 & z_1 + z_3 \end{bmatrix} = \begin{bmatrix} 1 + \frac{4}{3} & 1 \\ 1 & 1 + \frac{5}{2} \end{bmatrix}$$



$$[Z]_{2 \times 2} = \begin{bmatrix} 7/3 & 1 \\ 1 & 7/2 \end{bmatrix}$$

Method - II:

To find z_{11} :

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

From the n/w

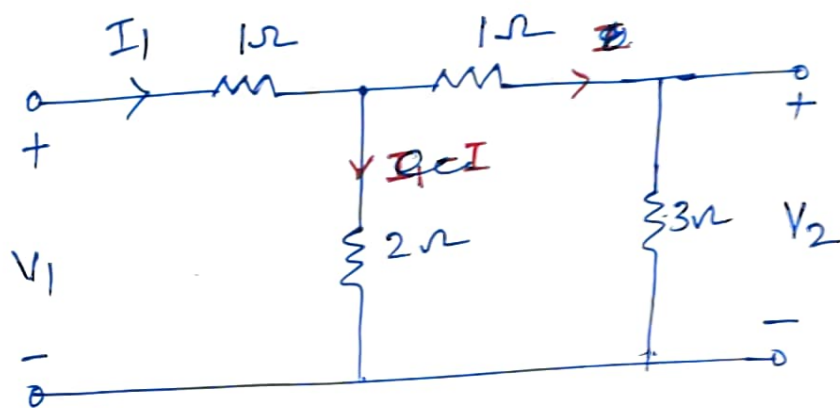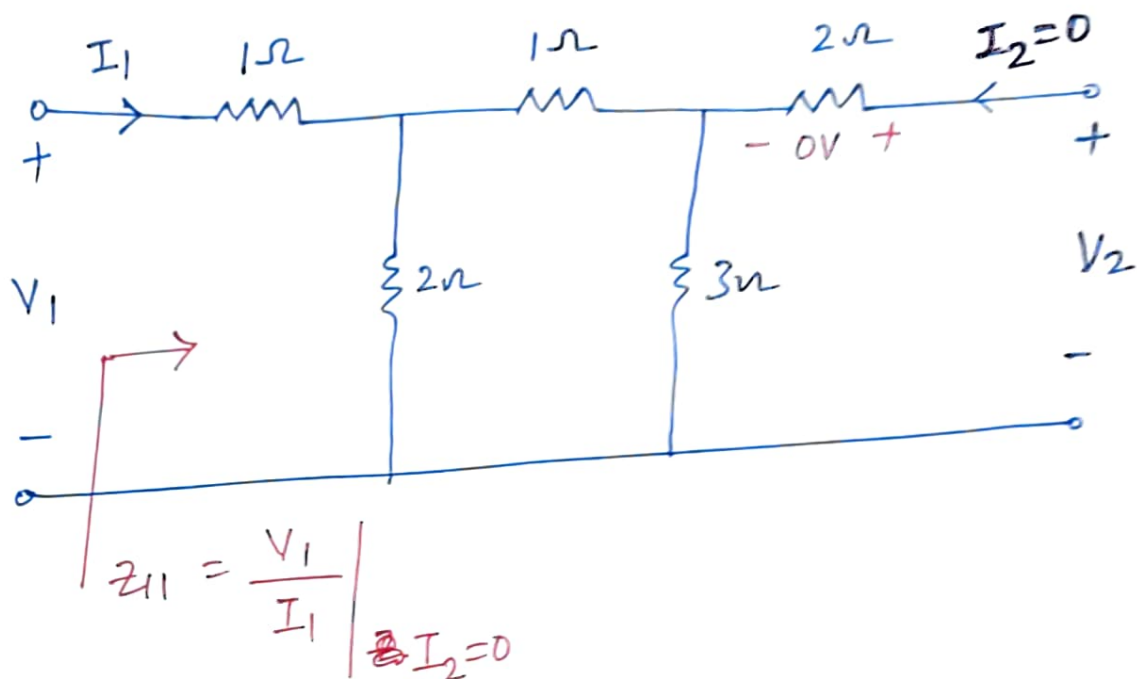


1Ω in series with $3\Omega \Rightarrow 1\Omega$ series 3Ω
 $= 4\Omega$

& $4\Omega \parallel 2\Omega$ so we can conclude that.

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = (4 \parallel 2) + 1 = \frac{8}{6} + 1 = \frac{4}{3} + 1 = \frac{7}{3} \Omega.$$


$$\therefore Z_{11} = \frac{7}{3} \Omega$$

(ii) To find Z_{22} :

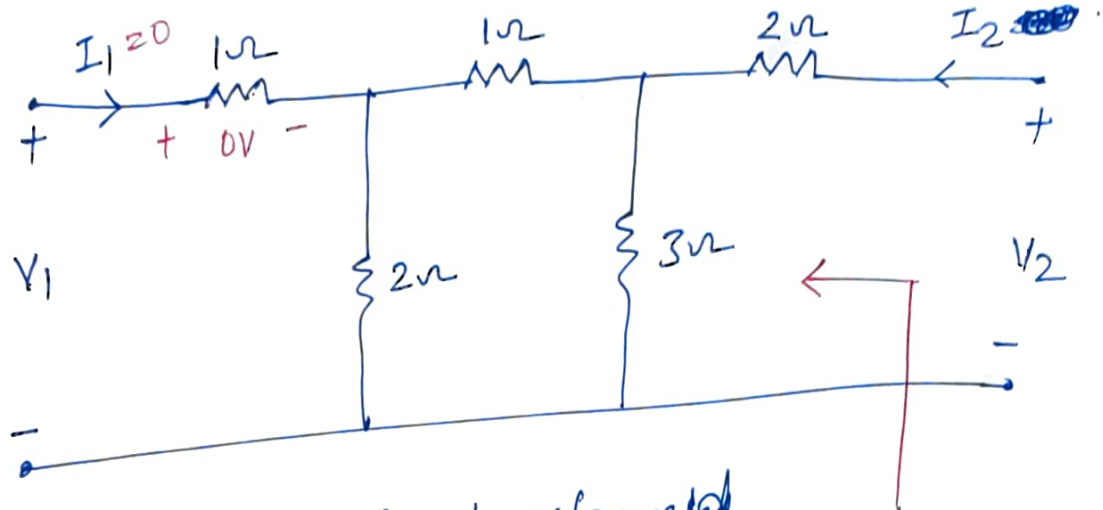

The above n/w is transformed as follows.

$$Z_{22} = \frac{V_2}{I_2} \bigg|_{I_1 = 0}$$

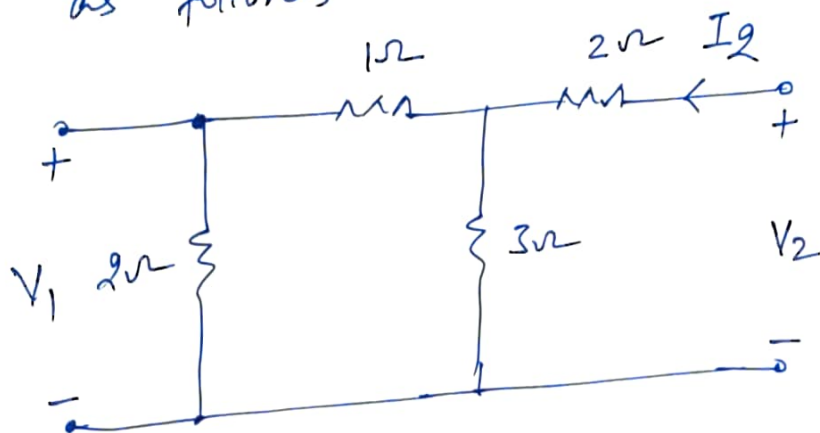


$$\frac{V_2}{I_2} = Z_{22} = [(2\Omega + 1\Omega) \parallel 3\Omega] + 2$$

$$= (3 \parallel 3) + 2 = \frac{3}{2} + 2 = \frac{7}{2} \Omega$$


$$\therefore Z_{22} = \frac{V_2}{I_2} = \frac{7}{2} \Omega$$

(ii) To find Z_{12}

$$Z_{12} = \frac{V_1}{I_2} \bigg|_{I_1 = 0}$$

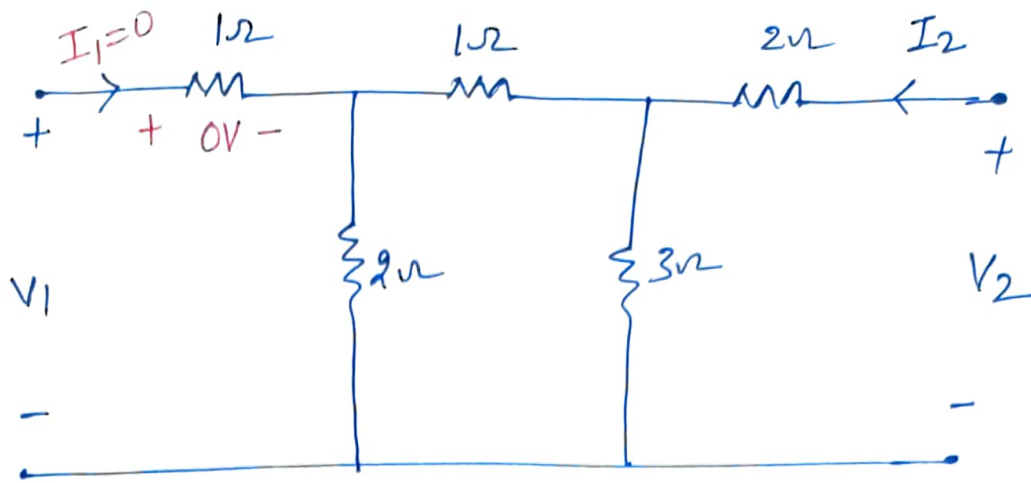

The above ckt will be transformed as.

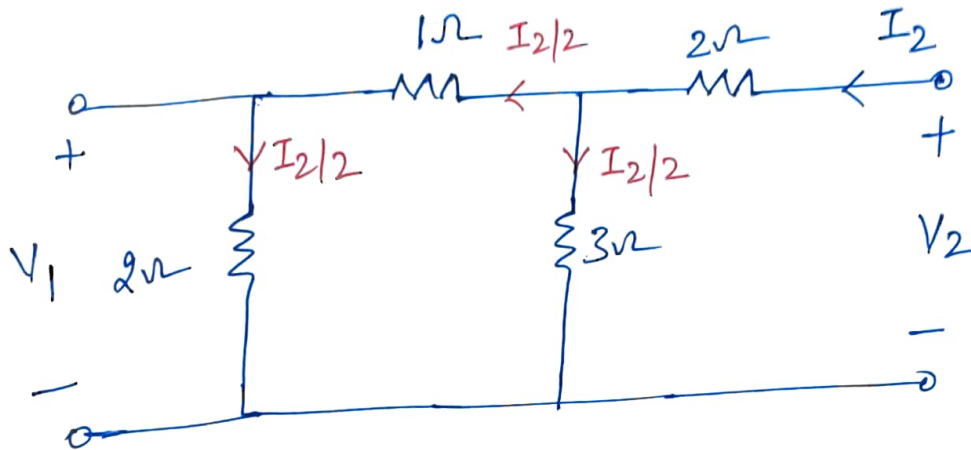

Here $(2\Omega + 1\Omega) \parallel 3\Omega$

$\Rightarrow 3\Omega \parallel 3\Omega$.

The current I_2 is divided equally as 3Ω & 3Ω are parallel and voltages across 3Ω & 3Ω are same

$$\text{Now } V_1 = (2) \left(\frac{I_2}{2} \right)$$



$$V_1 = I_2$$

$$Z_{12} = \frac{V_1}{I_2} \bigg|_{I_1=0} = 1 \Omega$$

$$\therefore Z_{12} = 1\Omega$$

To find Z_{21} :

$$Z_{21} = \frac{V_2}{I_1} \bigg|_{I_2=0}$$

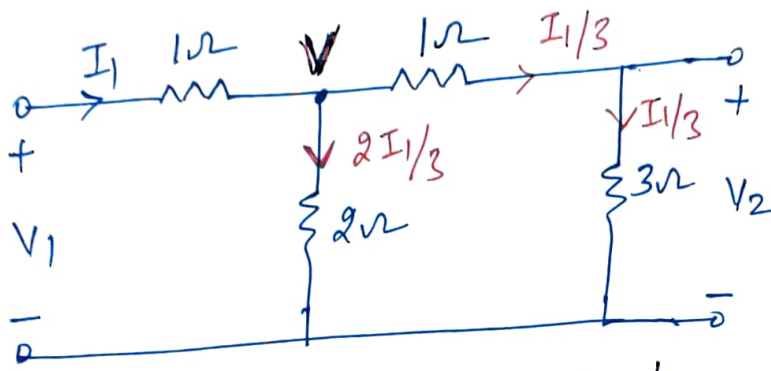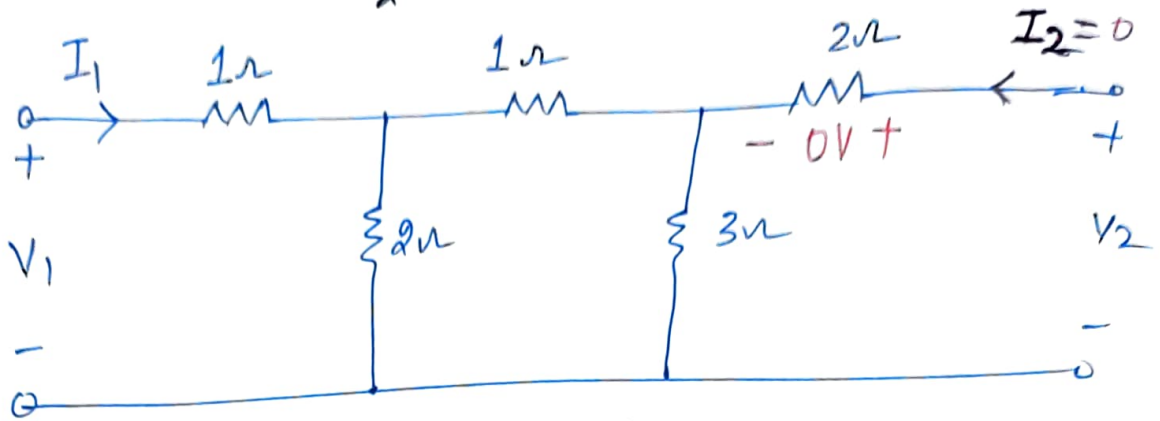

Apply nodal analysis at 'V'!

$$-I_1 + \frac{V}{2} + \frac{V}{4} = 0$$

$$\frac{V}{4} = \frac{I_1}{3} \rightarrow (2)$$

$$\frac{3V}{4} = I_1$$

$$\frac{V}{2} = \frac{2I_1}{3} \rightarrow (1)$$

Now $V_2 = (3) \left(\frac{I_1}{3} \right) = I_1$

$$V_2 = I_1$$


$$Z_{21} = \frac{V_2}{I_1} \bigg|_{I_2=0} = 1\Omega$$

$$\therefore Z_{21} = 1\Omega$$


Lecture - 4 :

Z -parameter^{me} of Symmetric Lattice Network :

Symmetric Lattice Network :

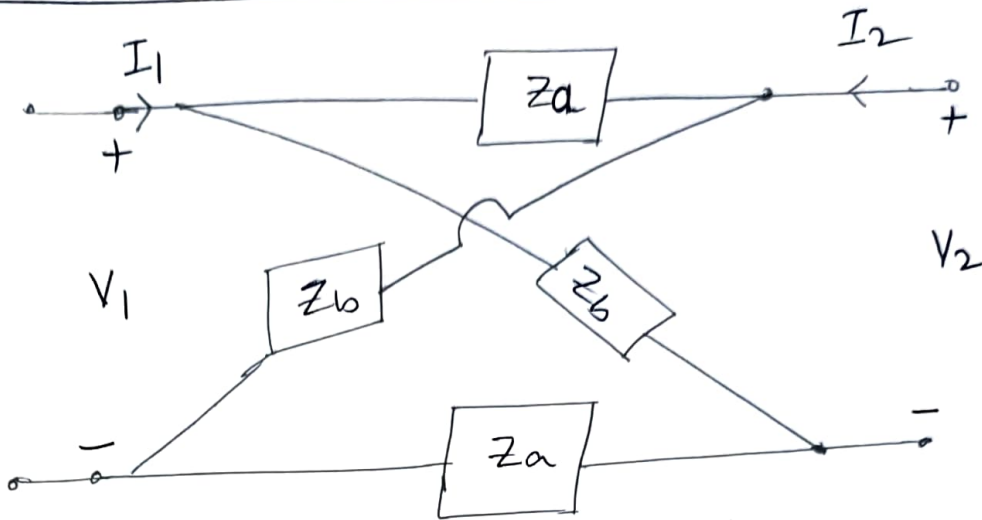

modified figure of the above n/w.

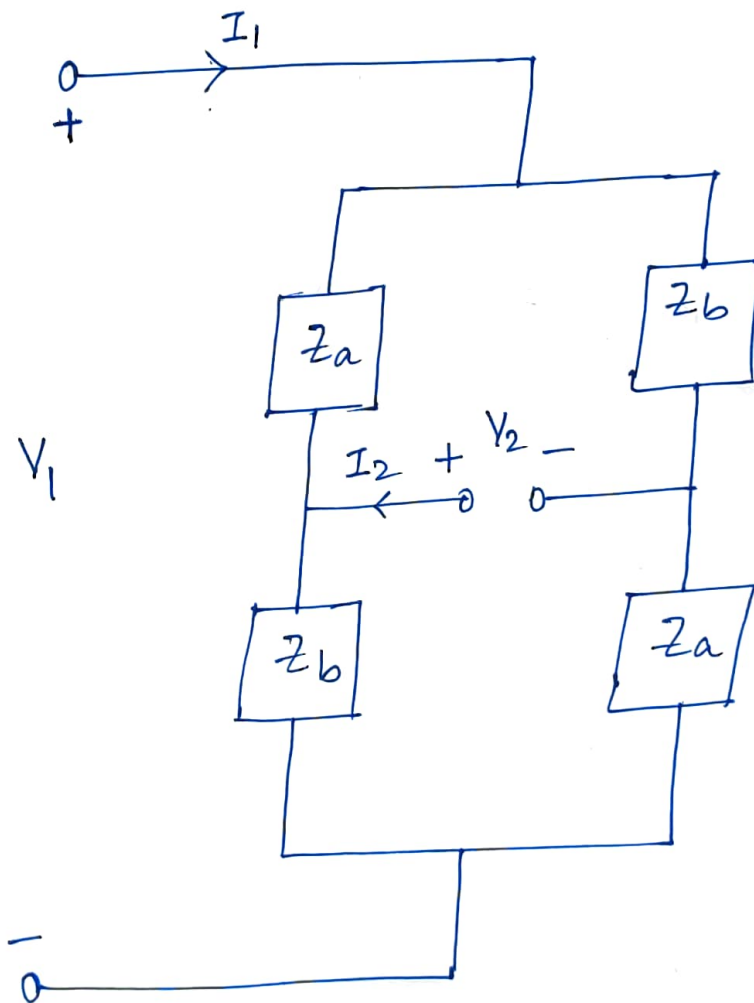

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0.4}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0.4}$$

Here o/p is open ckt

Here i/p is open ckt

for calc. of Z_{11} & Z_{21} ckt will be same:


The modified ckt is as follow

→ Current will be equally divided because 2 impedance is same in both paths i.e. $(Z_1 + Z_2)$.

Applying KVL in 'ABCD' loop.

$$V_1 - \frac{Z_a I_1}{2} - \frac{Z_b I_1}{2} = 0$$
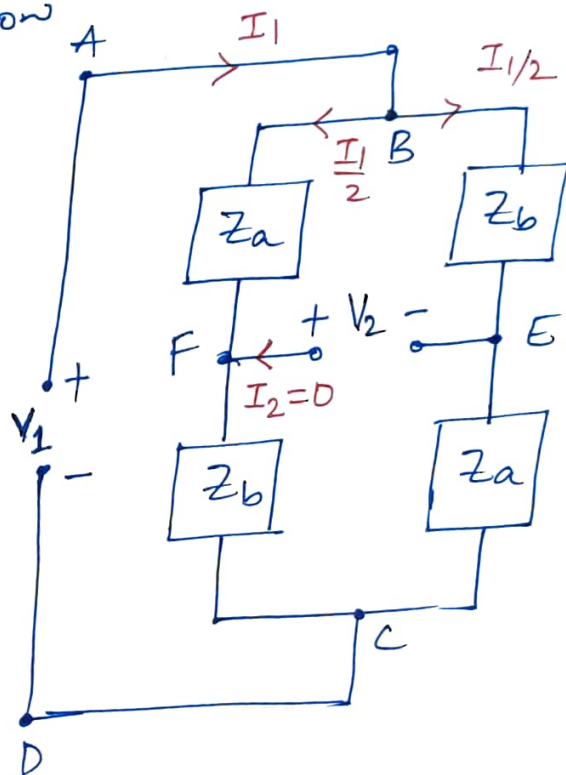
$$V_1 = \left[\frac{Z_a + Z_b}{2} \right] I_1$$



$$Z_{11} = \frac{V_1}{I_1} = \frac{Z_a + Z_b}{2}$$

Applying KVL in 'BEFB' loop

$$V_2 + \frac{Z_a I_1}{2} - \frac{Z_b I_1}{2} = 0$$



$$V_2 = \left[\frac{Z_b - Z_a}{2} \right] I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{Z_b - Z_a}{2}$$

for calc z_{12} & z_{22} ckt will be same :

The ckt will be transformed as

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} ; z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

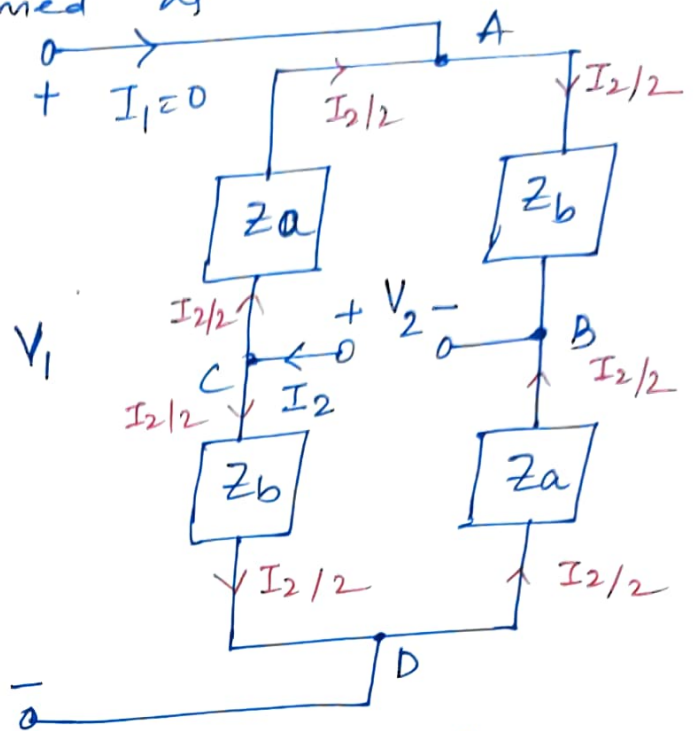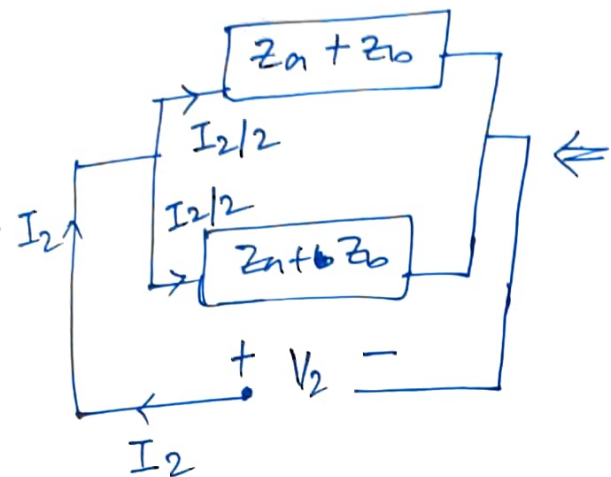

Here I_2 will be divided equally because of same impedance value.

Applying KVL in 'ABCA' loop

$$V_2 - \frac{Z_a I_2}{2} - \frac{Z_b I_2}{2} = 0$$

$$V_2 = \left(\frac{Z_a + Z_b}{2} \right) I_2$$

$$z_{22} = \frac{V_2}{I_2} = \frac{Z_a + Z_b}{2}$$

Applying KVL in 'ACDA' loop

$$\frac{Z_a I_2}{2} - \frac{Z_b I_2}{2} + V_1 = 0$$

$$V_1 = \left(\frac{Z_b - Z_a}{2} \right) I_2$$


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \left(\frac{z_b - z_a}{2} \right)$$

$$\therefore z_{12} = \left(\frac{z_b - z_a}{2} \right)$$

\therefore finally the z -parameters of symmetrical lattice network is given as

$$\begin{bmatrix} z \\ 2 \times 2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}_{2 \times 2} = \begin{bmatrix} \left(\frac{z_a + z_b}{2} \right) & \left(\frac{z_b - z_a}{2} \right) \\ \left(\frac{z_b - z_a}{2} \right) & \left(\frac{z_a + z_b}{2} \right) \end{bmatrix}_{2 \times 2}$$

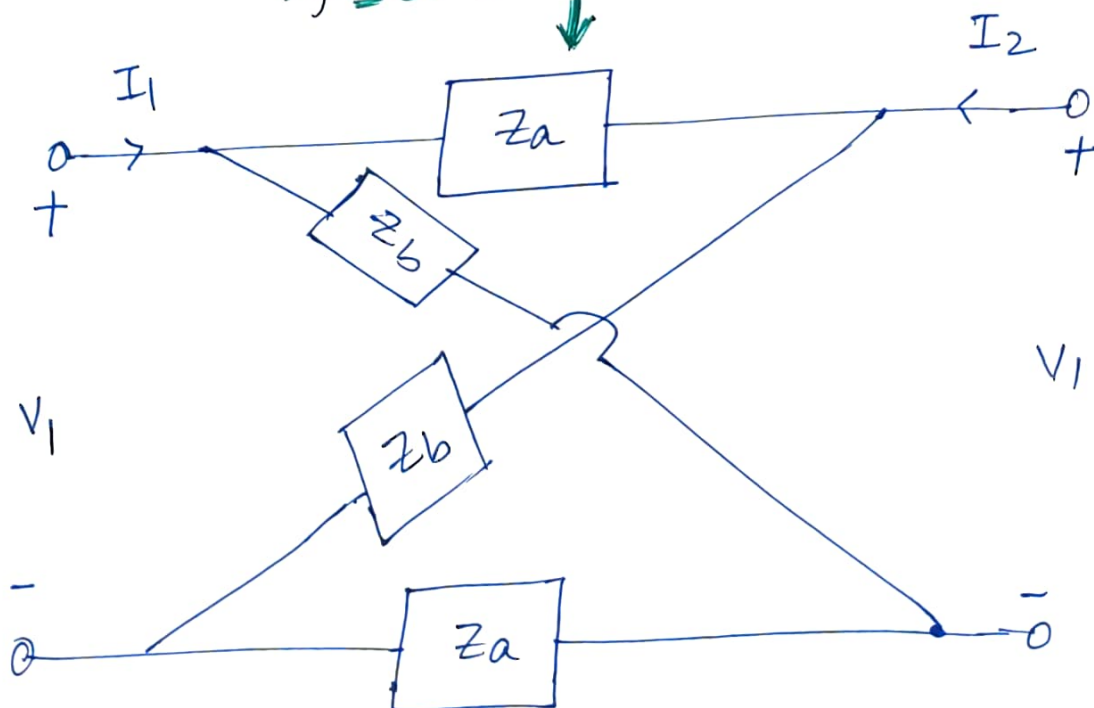Remember the result
for the following
symmetrical lattice network



Lecture - 5

Introduction To Y-Parameters :

Y-parameters (or) Admittance Parameters :

$$I_1 = y_{11} V_1 + y_{12} V_2 \longrightarrow \textcircled{1} : \text{I/P KCL}$$

$$I_2 = y_{21} V_1 + y_{22} V_2 \longrightarrow \textcircled{2} : \text{O/P KCL}$$

$$I_1 = f(V_1, V_2)$$

$$I_2 = f(V_1, V_2)$$

Independent variables = V_1, V_2

Dependent variables = I_1, I_2

Condition for existence of Y-parameters :

1. V_1 & V_2 should be independent from each other

2. which means V_2 cannot be ~~derived~~ ^{dependent} from V_1 on

$$V_1 \text{ i.e., } V_2 = \alpha V_1 \text{ (or) } V_1 = \alpha V_2$$

where ($\alpha = \text{constant}$)

Example: Consider a ^{ident} transformer with $n:1 = 4:5$. find


Y-parameters of this transformer.

Sol

Here

$$\frac{V_1}{V_2} = \frac{n}{1} = \frac{4}{5}$$
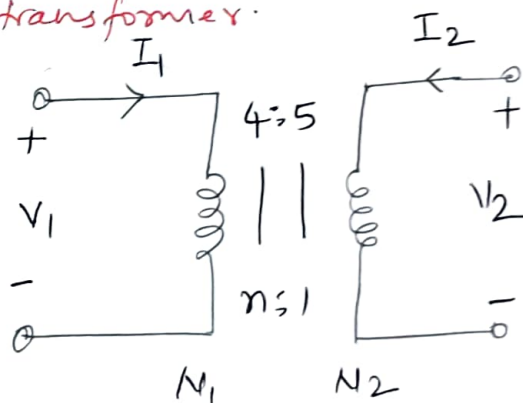
$$-\frac{I_2}{I_1} = \frac{n}{1} = \frac{4}{5}$$



Nearly $V_1 = \frac{4}{5} V_2 \Rightarrow V_1 \& V_2$ are dependent variables.

In this case Y -parameters of this transformer does not exist.

$\therefore Y$ -parameters does not exist for ideal transformer

Y -parameter (or) Admittance Model:

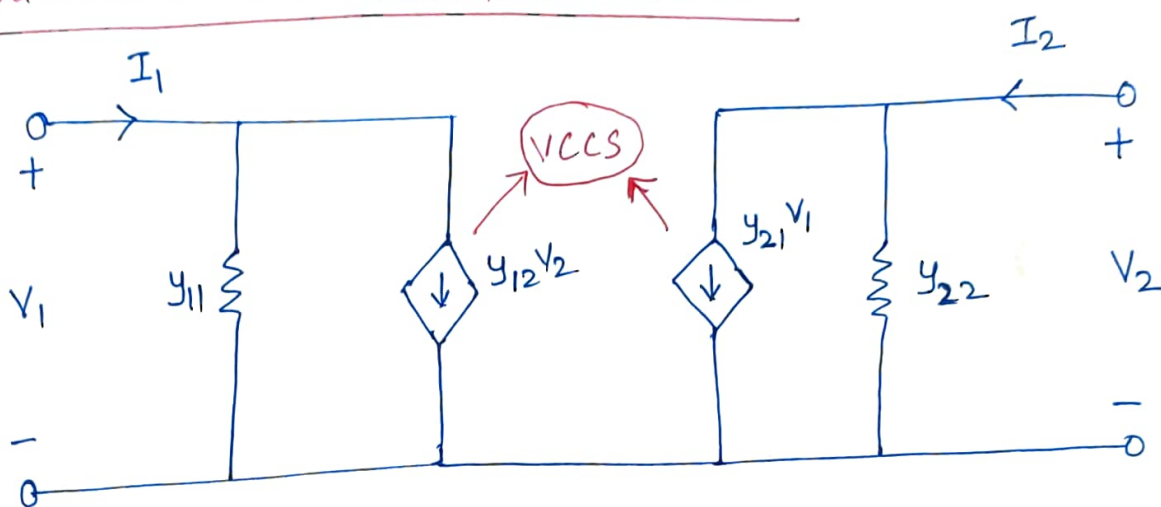


fig: Admittance model:

Matrix form of Y -parameter model:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}_{2 \times 1} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}_{2 \times 2} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}_{2 \times 1}$$

$$\begin{bmatrix} I \end{bmatrix}_{2 \times 1} = \begin{bmatrix} Y \end{bmatrix}_{2 \times 2} \begin{bmatrix} V \end{bmatrix}_{2 \times 1}$$

$$\begin{bmatrix} Y \end{bmatrix}_{2 \times 2} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \Rightarrow \text{Admittance matrix.}$$

$$\Delta y = y_{11}y_{22} - y_{21}y_{12} = \text{Determinant of } Y.$$

$$\text{Adj } Y = \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix} = \text{Adjoint of } Y\text{-matrix.}$$

$$[Y]^{-1} = \frac{\text{Adj } Y}{\Delta y} = \frac{1}{\Delta y} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix} \Rightarrow \text{Inverse of } Y \text{ matrix}$$

Relation b/w Y parameter matrix & Z-parameter matrix:


1. $[Z] = [Y]^{-1} \rightarrow$ Remember this result

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{y_{22}}{\Delta y} & \frac{-y_{12}}{\Delta y} \\ \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{bmatrix} \rightarrow \text{Donot remember this result}$$

2. $[Y] = [Z]^{-1} \rightarrow$ Remember this result

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix} \rightarrow \text{Do not remember this result}$$

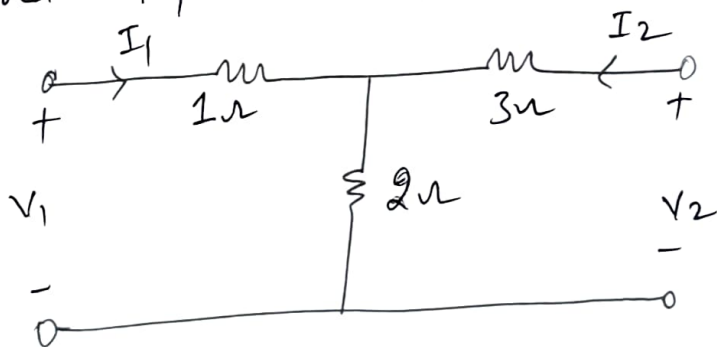Example: Find Y-parameters for the following T n/w.



sol. We have


$$Z_1 = 2\Omega; Z_2 = 1\Omega; Z_3 = 3\Omega$$

We know that

$$[Z] = \begin{bmatrix} Z_1 + Z_2 & Z_1 \\ Z_1 & Z_1 + Z_3 \end{bmatrix}$$

$$[Z]_{2 \times 2} = \begin{bmatrix} 3 & 2 \\ 2 & 5 \end{bmatrix}_{2 \times 2}$$

But $[Y] = [Z]^{-1}$

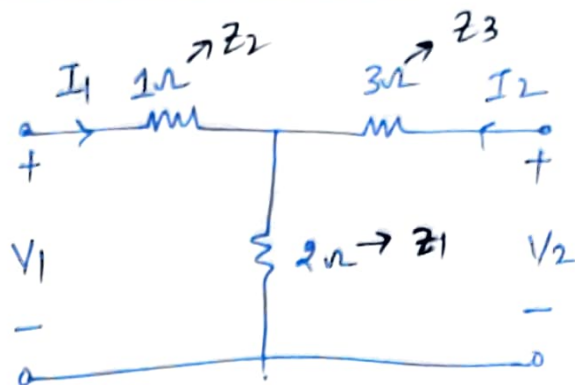

$$\Delta Z = |5 - 4| = 1$$

$$\text{Adj } Z = \begin{bmatrix} 5 & -2 \\ -2 & 3 \end{bmatrix}$$

$$Z^{-1} = \frac{\text{Adj } Z}{\Delta Z}$$

$$\therefore [Y] = Z^{-1} = \frac{1}{1} \begin{bmatrix} 5 & -2 \\ -2 & 3 \end{bmatrix} = \begin{bmatrix} 5 & -2 \\ -2 & 3 \end{bmatrix}$$

$$\therefore [Y]_{2 \times 2} = \begin{bmatrix} 5 & -2 \\ -2 & 3 \end{bmatrix}$$

$$[Y] = [Z]^{-1} = \frac{1}{11} \begin{bmatrix} 5 & -2 \\ -2 & 3 \end{bmatrix} = \begin{bmatrix} 5/11 & -2/11 \\ -2/11 & 3/11 \end{bmatrix}$$

$$\therefore [Y]_{2 \times 2} = \begin{bmatrix} 5/11 & -2/11 \\ -2/11 & 3/11 \end{bmatrix}_{2 \times 2}$$

$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$ = Driving point i/p admittance when o/p is short circuit

$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$ = Transfer point i/p admittance when i/p is short circuit


$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$ = Transfer o/p admittance when o/p is short circuit.

$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$ = Driving point o/p admittance when i/p is short circuit.

NOTE: 'y' parameters are called as short circuit parameters.


To find y_{11} :

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

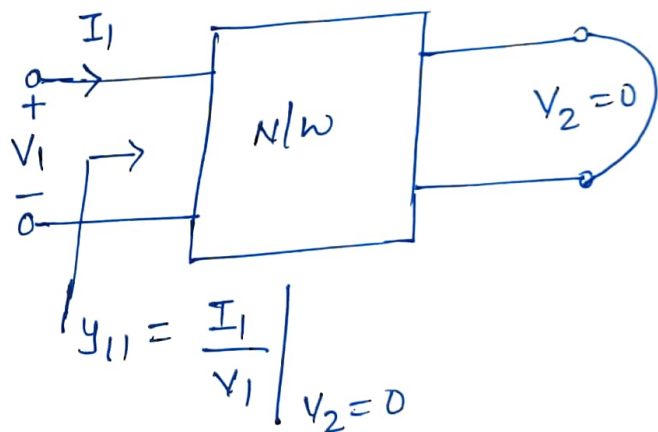


To find y_{22} :

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

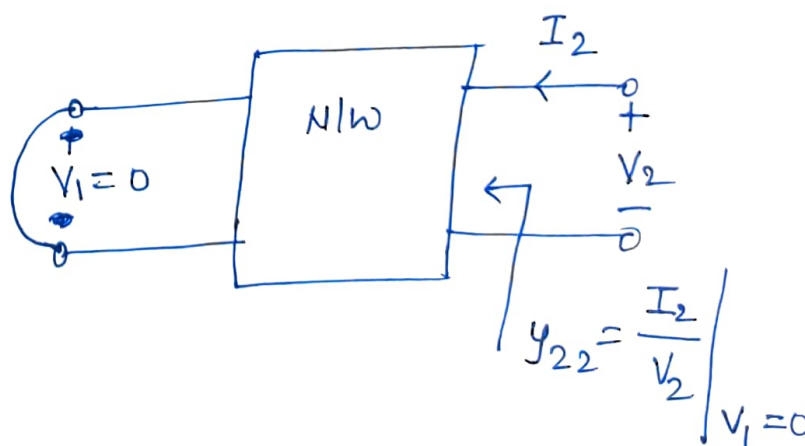

Note: We cannot represent the figure for calculating transfer i/p & o/p ~~admittance~~ i.e. y_{12} & y_{21} admittances.

UNCONDITIONAL I/p Admittance:

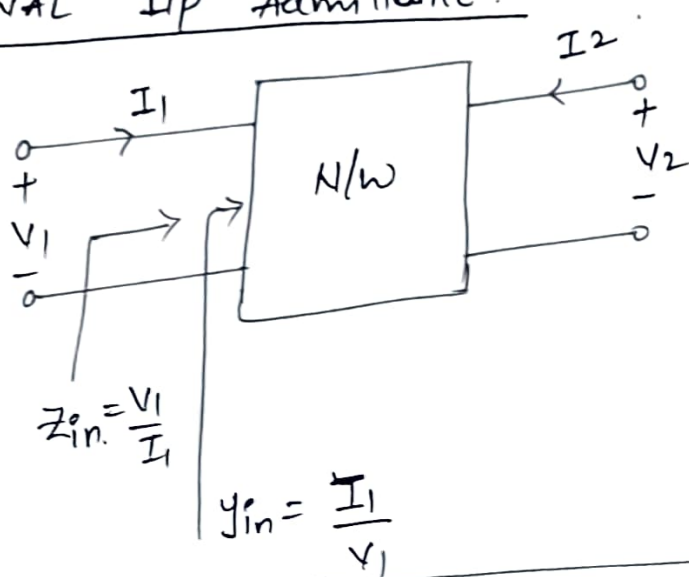

$$Z_{in} = \frac{1}{y_{in}}$$

$$\text{Unconditional i/p admittance } (y_{in}) = \frac{I_1}{V_1}$$

NOTES:

1. All the y -parameters $y_{11}, y_{12}, y_{21}, y_{22}$ are called conditional admittances, because they are obtained by imparting the condition i.e. either $V_1 = 0$ or $V_2 = 0$.

2. y_{11} is different from y_{in} .

3. $y_{11} = \text{Conditional Driving point i/p admittance}$

$y_{in} = \text{unconditional i/p admittance}$

* Important Concept



Always

$$Z_{11} \neq \frac{1}{y_{11}}$$

i.e.

$$Z_{11} \neq \frac{1}{y_{11}}$$

Proof

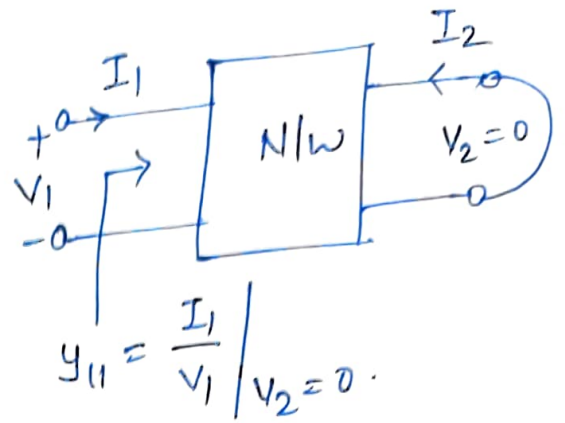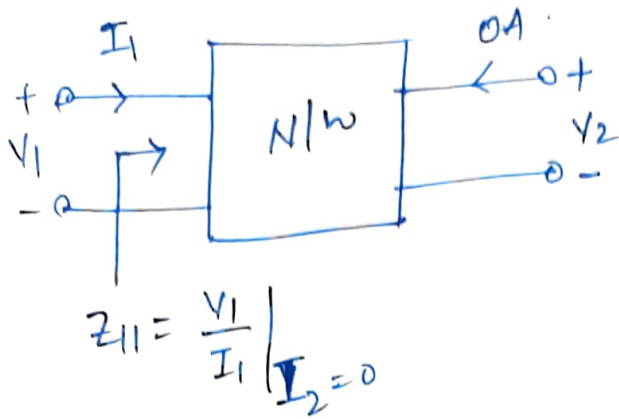

Clearly we can say that $Z_{11} \neq \frac{1}{Y_{11}}$. As the conditions imparted in both cases are different i.e. $I_2 = 0$ & $V_2 = 0$.

$\therefore \boxed{Y_{11} \neq \frac{1}{Z_{11}}}$. Hence proved.

NOTE: But we can say that

$$\boxed{Z_{in} = \frac{1}{Y_{in}}}$$

Z_{in} = unconditional i/p impedance

Y_{in} = unconditional i/p admittance.